

# Lecture 8

## The Electric Current and the resistance


- **Electric current and Ohm's law**
- **The Electromotive Force and Internal Resistance**
- **Electrical energy and thermal energy**
- **Resistors in series.**
- **Resistors in parallel.**
- **Kirchhoff's Laws and its applications.**
- **Charging and Discharging Processes in RC**

## Electric current and Ohm's law

The **current is defined as the flow of the charge.**

- The current is the rate at which charge flows through a surface of area  $A$ ,
- If  $\Delta Q$  is the amount of charge that passes through this area in a time interval  $\Delta t$ , the average current  $I_{av}$  is equal to the charge that passes through  $A$  per unit time:

$$I_{av} = \frac{\Delta Q}{\Delta t}$$

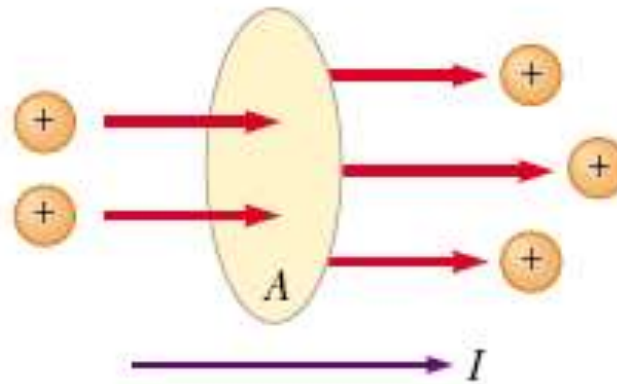

The SI unit of current is the ampere (A): That is, 1 A of current is equivalent to 1 C of charge passing through the surface area in 1 s.

$$1 \text{ A} = \frac{1 \text{ C}}{1 \text{ s}}$$

# The current density

- Consider a conductor of cross-sectional area  $A$  carrying a current  $I$ . The current density  $\mathbf{J}$  in the conductor is defined as the current per unit area. Because the current  $I = nqv_dA$ , the current density is

**The current density** 
$$\mathbf{J} \equiv \frac{I}{A} = nqv_d$$

where  $J$  has SI units of  $\text{A}/\text{m}^2$ .

A current density  $\mathbf{J}$  and an electric field  $\mathbf{E}$  are established in a conductor whenever a potential difference is maintained across the conductor, the current density is proportional to the electric field:

$$\mathbf{J} = \sigma \mathbf{E}$$

$\sigma$  is called the conductivity of the conductor.

# Ohm's Law

Ohm's law states that:

for many materials the ratio of the current density to the electric field is a constant  $\sigma$  that is independent of the electric field producing the current.

$$J = \sigma E = \sigma \frac{\Delta V}{\ell}$$

Because  $J = I/A$ , we can write the potential difference as

$$\Delta V = \frac{\ell}{\sigma} J = \left( \frac{\ell}{\sigma A} \right) I = RI$$

The quantity  $R = \ell/\sigma A$  is called the **resistance** of the conductor.

$$R \equiv \frac{\Delta V}{I}$$

# Ohm's Law

In order for a current  $I$  to flow there must be a potential difference, or voltage  $V$ , across the conducting material. We define the resistance,  $R$ , of a material to be:

$$R = \frac{V}{I}$$

**The unit of resistance is Ohms ( $\Omega$ ):  $1 \Omega = 1 \text{ V/A}$**

For many materials,  $R$  is constant, the material is said to be ohmic, and we write Ohm's Law:

$$V = IR$$

$$R = \frac{V}{I}$$

The inverse of conductivity is resistivity  $\rho$ . Where  $\rho$  has the units ( $\Omega \cdot m$ ). Because

$$R = l / \sigma \cdot A = \rho l / A$$

$$R = \rho \frac{\ell}{A}$$

**Table 5.1 Values of Resistivity of Materials**

<b>Material</b>	<b>Resistivity (<math>\Omega \cdot \text{m}</math>)</b>
<b>Metals:</b>	
Silver	$1.47 \times 10^{-8}$
Copper	$1.72 \times 10^{-8}$
Gold	$2.44 \times 10^{-8}$
Aluminum	$2.63 \times 10^{-8}$
Tungsten	$5.51 \times 10^{-8}$
Steel	$20 \times 10^{-8}$
Lead	$22 \times 10^{-8}$
Mercury	$95 \times 10^{-8}$
<b>Semiconductors:</b>	
Pure carbon	$3.5 \times 10^{-5}$
Pure germanium	0.60
Pure silicon	2300
<b>Insulators:</b>	
Amber	$5 \times 10^{14}$
Mica	$10^{11} - 10^{15}$
Teflon	$10^{16}$
Quartz	$7.5 \times 10^{17}$

# Electromotive Force

- When the current in the circuit is constant in magnitude and direction and is called **direct current DC**.
- A battery is called a source of electromotive force or, *emf*.
- **The emf of a battery is the maximum possible voltage that the battery can provide between its terminals.**
- When an electric potential difference exists between two points, the source moves charges from the lower potential to the higher.
  - What makes charges flow in circuits?
    - Potential difference  $\Delta V$
    - Source of charges
  - This is what the EMF provides
    - NB: EMF=Electromotive force but it's not a force!!!





# The internal resistance

- The resistance of the battery is called **internal resistance**  $r$ .
- $I$  is the current in the circuit,  $I_r$  is the current through the resistor, emf is  $\varepsilon$
- The terminal voltage of the battery

$$\Delta V = V_b - V_a \text{ is}$$

$$\Delta V = \varepsilon - I_r r$$

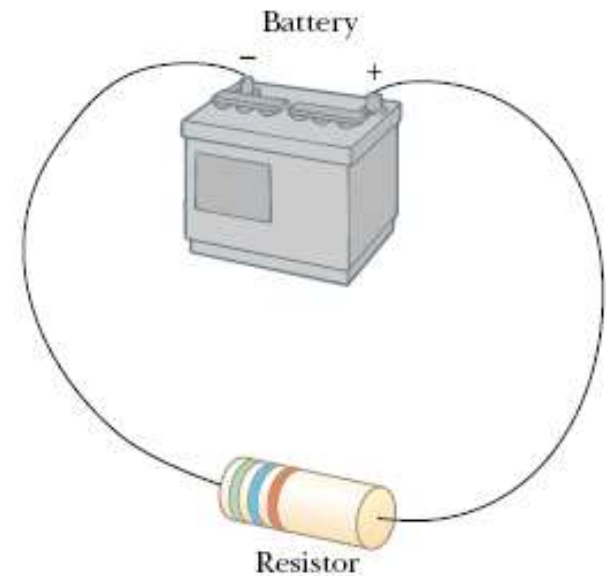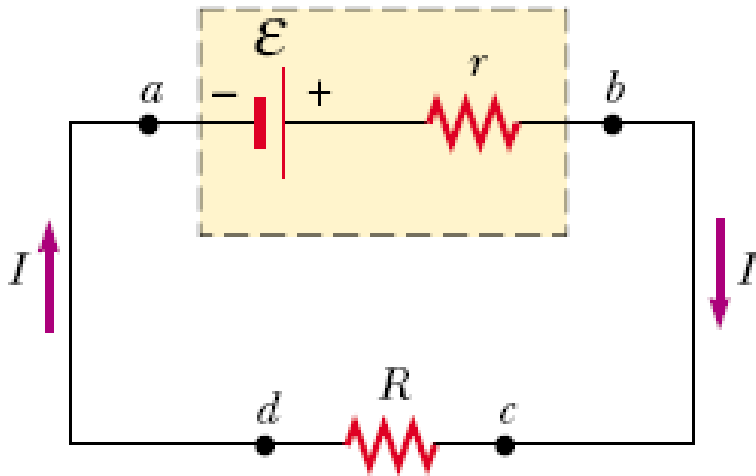

## Electrical energy and thermal energy.

- The resistor represents a *load* on the battery because the battery must supply energy to operate the device.
- The potential difference across the load resistance is
- $\Delta V = \mathbf{IR}$  and

$$I = \frac{\mathbf{\varepsilon}}{R + r}$$

- The total power output  $I\varepsilon$  of the battery is delivered to the external load resistance in the amount  $I^2R$  and to the internal resistance in the amount  $I^2r$ .

$$I\varepsilon = I^2R + I^2r$$

# Electrical Power and Electrical Work

All electrical circuits have three parts in common.

1. A voltage source.
  2. An electrical device
  3. Conducting wires.
- **The work done (W) by a voltage source is equal to the work done by the electrical field in an electrical device,**

$$1. \text{ Work} = \text{Power} \times \text{Time.}$$

**The electrical potential** is measured in **joules/coulomb** and a quantity of **charge is measured in coulombs**, so the **electrical work is measure in joules**.

A **joule/second** is a unit of power called the **watt**.

$$2. \text{ Power} = \text{current} \times \text{potential}$$

Or, 
$$P = I V = I^2 R$$

- **Energy = Power / Time**

## Example 28.1 Terminal Voltage of a Battery

A battery has an emf of 12.0 V and an internal resistance of 0.05  $\Omega$ . Its terminals are connected to a load resistance of 3.00  $\Omega$ .

**(A)** Find the current in the circuit and the terminal voltage of the battery.

**Solution** Equation 28.3 gives us the current:

$$I = \frac{\mathcal{E}}{R + r} = \frac{12.0 \text{ V}}{3.05 \Omega} = 3.93 \text{ A}$$

and from Equation 28.1, we find the terminal voltage:

$$\Delta V = \mathcal{E} - Ir = 12.0 \text{ V} - (3.93 \text{ A})(0.05 \Omega) = 11.8 \text{ V}$$




- Calculate the power delivered to the load resistor of 3 ohm when the current in the circuit is 3.93 A.

**Solution** The power delivered to the load resistor is

$$\mathcal{P}_R = I^2 R = (3.93 \text{ A})^2 (3.00 \text{ } \Omega) = 46.3 \text{ W}$$
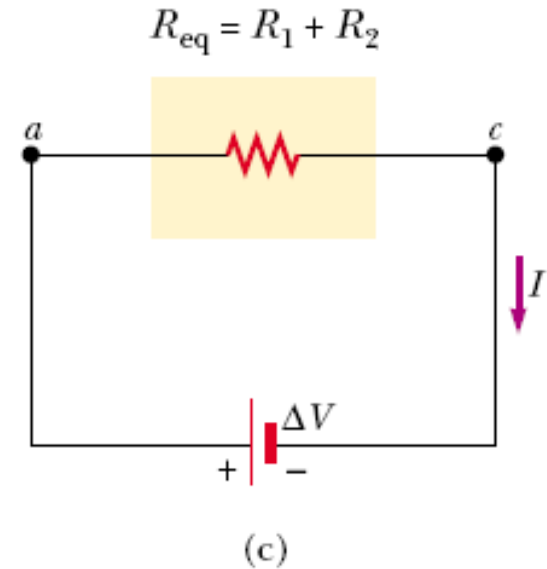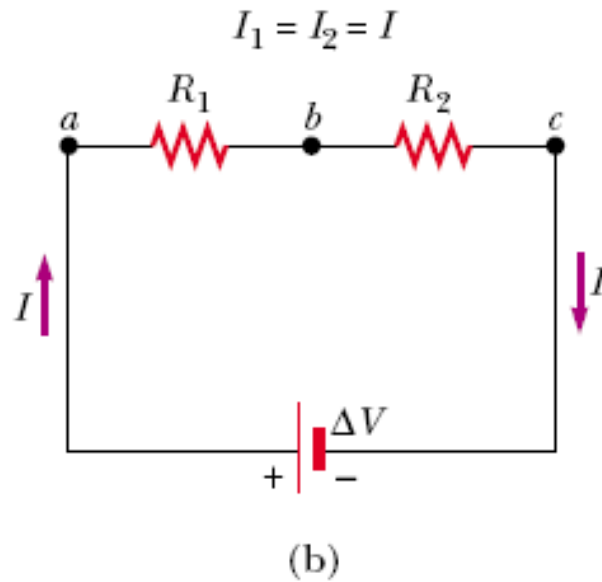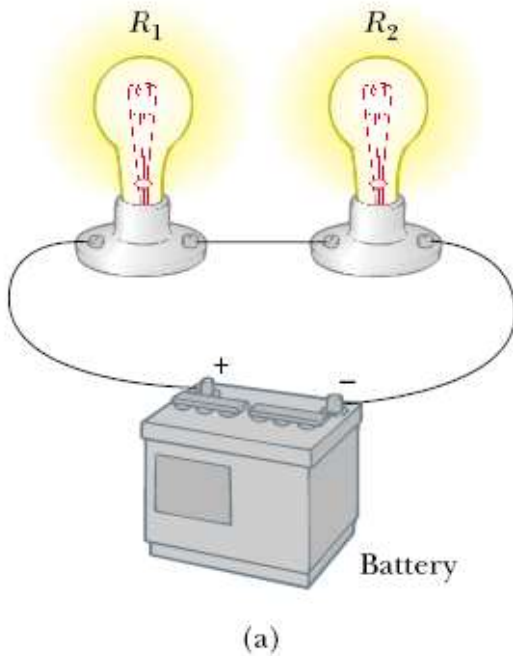
# Resistors in Series

- for a series combination of two resistors, the currents are the same in both resistors because the amount of charge that passes through  $R_1$  must also pass through  $R_2$  in the same time interval.



The potential difference across the battery is applied to the **equivalent resistance**  $R_{eq}$ :

$$\Delta V = IR_{eq}$$

## Resistors in Series

$$\Delta V = IR_{\text{eq}}$$


$$\Delta V = IR_{\text{eq}} = I(R_1 + R_2) \longrightarrow R_{\text{eq}} = R_1 + R_2$$

**The equivalent resistance of three or more resistors connected in series is**

$$R_{\text{eq}} = R_1 + R_2 + R_3 + \dots$$

**Problem 5.8.** Consider the series portion of a circuit shown in Fig. 5-4. The current in the circuit flows from *a* to *b* and is 2.3 A.

- (a) What is the equivalent resistance?
- (b) What is the voltage across the entire circuit? Which point, *a* or *b*, is at the higher potential?
- (c) What is the voltage across each resistor?

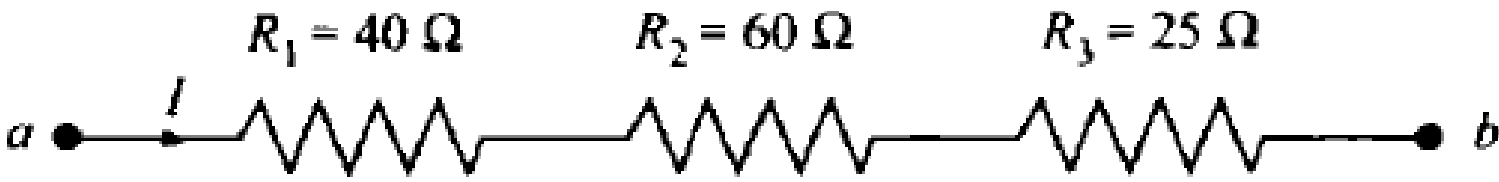

**Fig. 5-4**



**Problem 5.8.** Consider the series portion of a circuit shown in Fig. 5-4. The current in the circuit flows from  $a$  to  $b$  and is 2.3 A.

- What is the equivalent resistance?
- What is the voltage across the entire circuit? Which point,  $a$  or  $b$ , is at the higher potential?
- What is the voltage across each resistor?



### Solution

- The equivalent resistance is the sum of all the resistances, or  $R_{\text{eq}} = 40 + 60 + 25 = 125 \Omega$ .
- The voltage across the entire circuit is  $V_{\text{total}} = IR_{\text{eq}} = (2.3 \text{ A})(125 \Omega) = 288 \text{ V}$ . Since the current flows from  $a$  to  $b$ , and the electric field does positive work in pushing charges through the resistors, energy is lost as the charges move through. Thus the potential at  $a$  is higher (by 288 V) than the potential at  $b$ .
- The voltage across each resistor is  $IR_i$ . Thus  $V_1 = (2.3 \text{ A})(40 \Omega) = 92 \text{ V}$ ,  $V_2 = (2.3 \text{ A})(60 \Omega) = 138 \text{ V}$  and  $V_3 = (2.3 \text{ A})(25 \Omega) = 58 \text{ V}$ .

*Note.* Adding the voltages gives  $92 + 138 + 58 = 288 \text{ V}$ , which is the voltage we calculated in part(b).
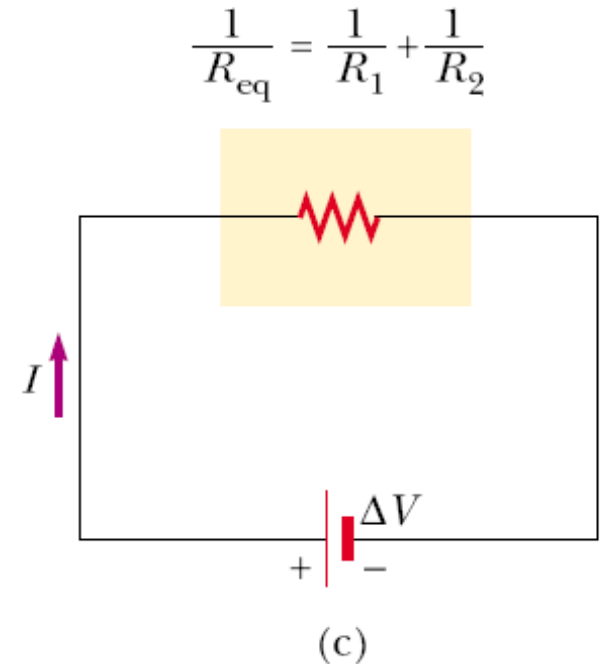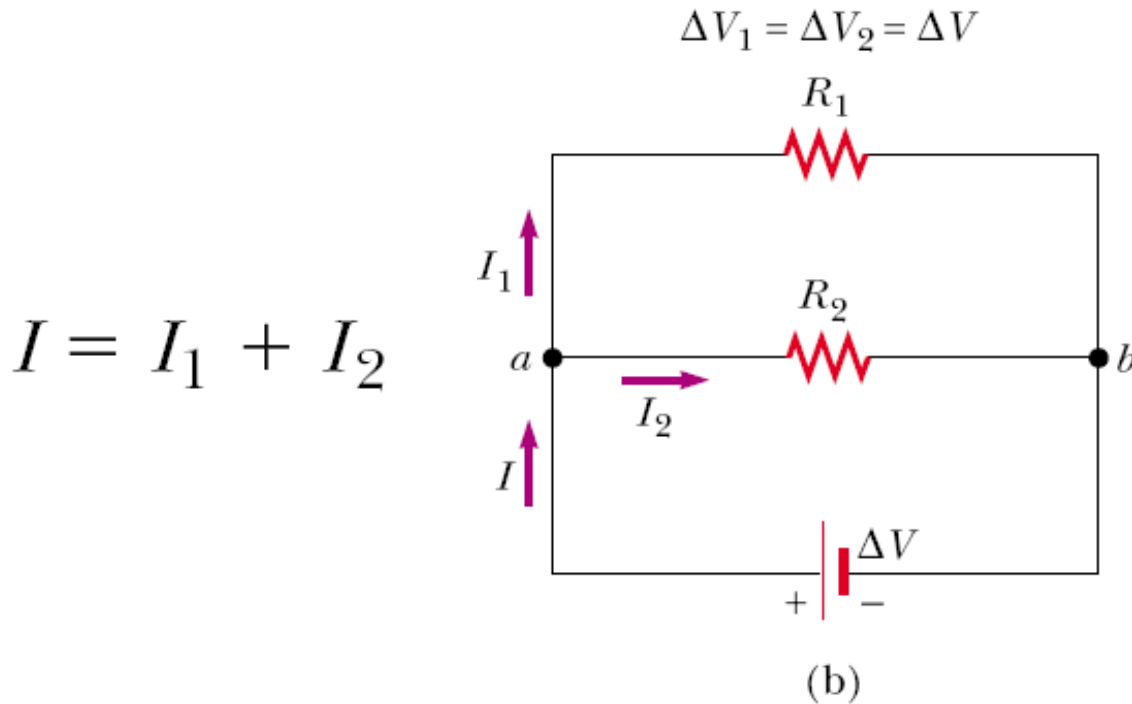
# Resistors in Parallel

- The current  $I$  that enters point  $a$  must equal the total current leaving that point:



When resistors are connected in parallel, the potential differences across the resistors **is the same**.

# Resistors in Parallel

- Because the potential differences across the resistors are the same, the expression
- $\Delta V = IR$  gives


$$I = I_1 + I_2 = \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2} = \Delta V \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{\Delta V}{R_{\text{eq}}}$$

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

the equivalent resistance

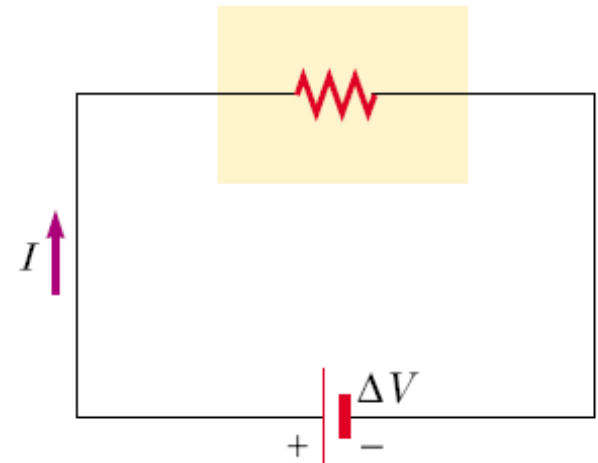
$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$



(c)

**Problem 5.9.** Three resistors are connected in parallel, as in Fig. 5-5. The potential difference between *a* and *b* is 75 V.


- (a) What is the equivalent resistance of this circuit?
- (b) What is the current flowing from point *a*?
- (c) What is the current in each resistor?

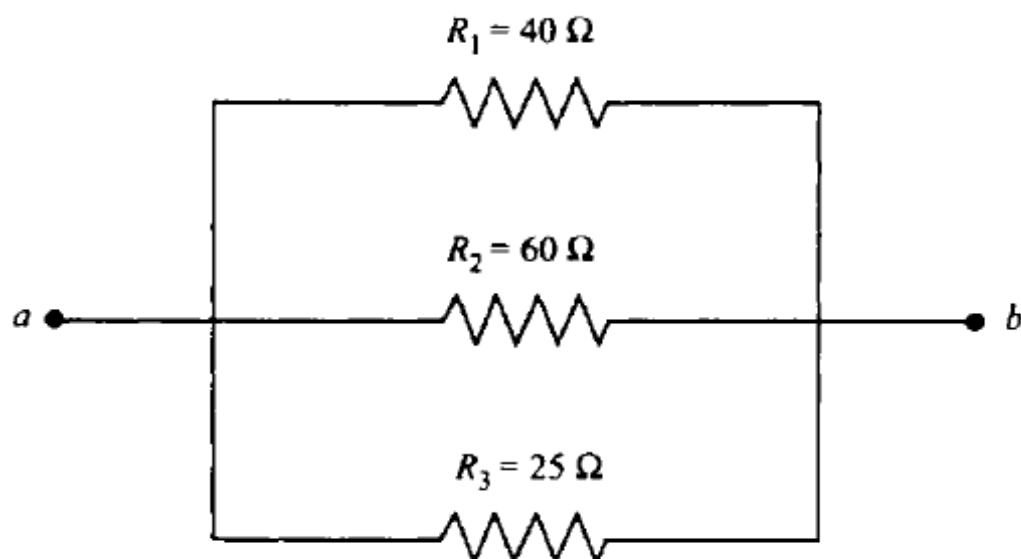

**Fig. 5-5**

**Problem 5.9.** Three resistors are connected in parallel, as in Fig. 5-5. The potential difference between  $a$  and  $b$  is 75 V.

- (a) What is the equivalent resistance of this circuit?
- (b) What is the current flowing from point  $a$ ?
- (c) What is the current in each resistor?

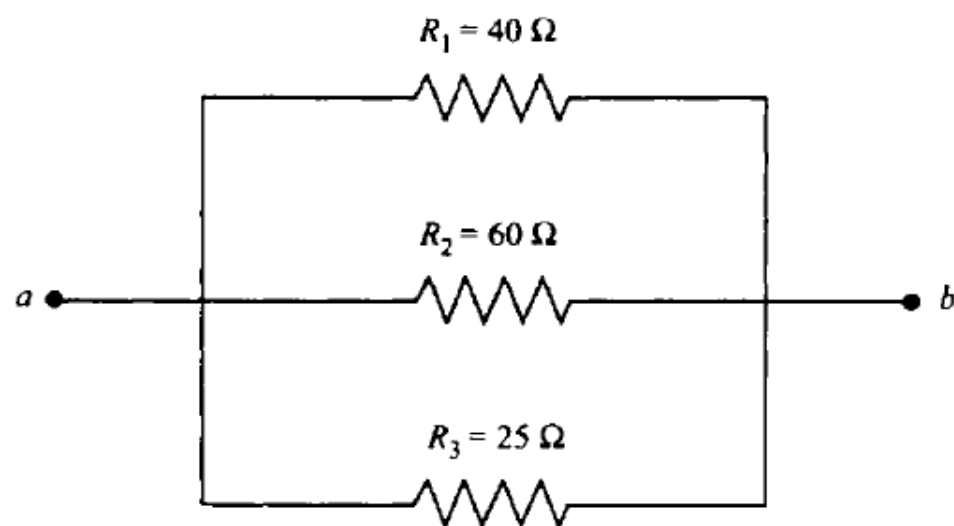


**Fig. 5-5**
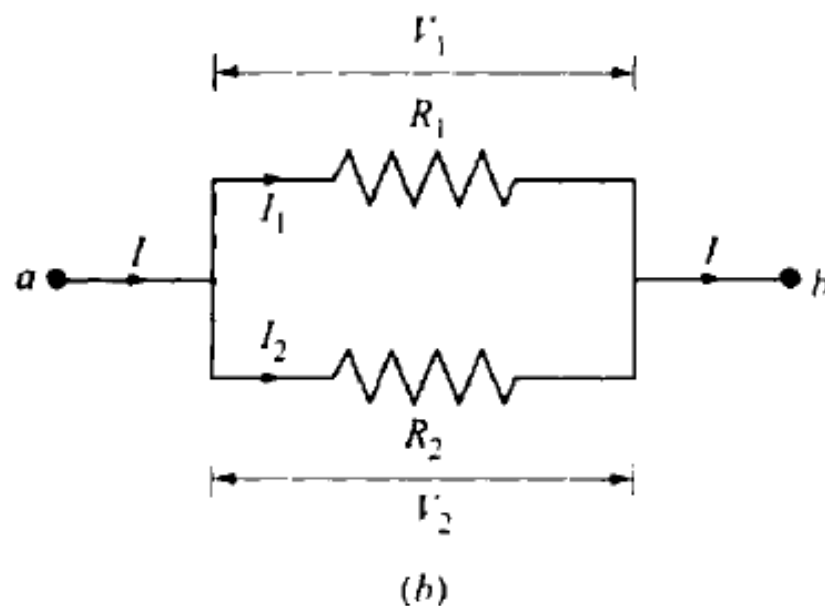
### Solution

- (a) The equivalent resistance is given by  $1/R_{\text{eq}} = \Sigma (1/R_i) = 1/40 + 1/60 + 1/25 = 0.817$ , or  $R_{\text{eq}} = 12.2 \Omega$ .
- (b) The total current is  $I_{\text{tot}} = V/R_{\text{eq}}$ . Thus  $I_{\text{tot}} = 6.13 \text{ A}$ .
- (c) The current in each resistor is  $I_i = V/R_i$ . Thus  $I_1 = (75 \text{ V})/(40 \Omega) = 1.88 \text{ A}$ ,  $I_2 = (75 \text{ V})/(60 \Omega) = 1.25 \text{ A}$ ,  $I_3 = (75 \text{ V})/(25 \Omega) = 3.0 \text{ A}$ . [The total current is  $1.88 + 1.25 + 3.0 = 6.13 \text{ A}$ , as in part(b).]

**Problem 5.20.** In the circuit segment of Fig. 5-2(b), the voltage across the circuit is 55V. If  $R_1 = 25 \Omega$  and  $R_2 = 35 \Omega$ , calculate (a) the current in each resistor; (b) the power dissipated in each resistor and (c) the power dissipated in the equivalent resistance. Compare the answer to this with the sum of the answers to (b).



**Solution**

(a) The voltage across each resistor is 55 V. Thus the current for each resistor is  $I = V/R$ . Then  $I_1 = (55 \text{ V})/(25 \Omega) = 2.2 \text{ A}$ , and  $I_2 = (55 \text{ V})/(35 \Omega) = 1.57 \text{ A}$ .

**Problem 5.20.** In the circuit segment of Fig. 5-2(b), the voltage across the circuit is 55V. If  $R_1 = 25 \Omega$  and  $R_2 = 35 \Omega$ , calculate (a) the current in each resistor; (b) the power dissipated in each resistor and (c) the power dissipated in the equivalent resistance. Compare the answer to this with the sum of the answers to (b).

### Solution

- (a) The voltage across each resistor is 55 V. Thus the current for each resistor is  $I = V/R$ . Then  $I_1 = (55 \text{ V})/(25 \Omega) = 2.2 \text{ A}$ , and  $I_2 = (55 \text{ V})/(35 \Omega) = 1.57 \text{ A}$ .
- (b) Since the voltage across each resistor is the same, the power in each resistor can be calculated using  $P = V^2/R$ . Thus  $P_1 = (55 \text{ V})^2/(25 \Omega) = 121 \text{ W}$ , and  $P_2 = (55 \text{ V})^2/(35 \Omega) = 86.4 \text{ W}$ . Alternatively, we could have used  $P = I^2R$ , using the current appropriate to each resistor. Then  $P_1 = (2.2 \text{ A})^2(25 \Omega) = 121 \text{ W}$ , and  $P_2 = (1.57 \text{ A})^2(35 \Omega) = 86.4 \text{ W}$ .
- (c) The equivalent resistance is  $R_{eq} = (25)(35)/(25 + 35) = 14.6 \Omega$ . The total power is therefore  $P_{tot} = (55)^2/14.6 = 207.4 \text{ W}$ . This equals the sum of  $P_1 + P_2 = 121 + 86.4$ .

# Kirchhoff's Rules

- The procedure for analyzing more complex circuits is greatly simplified if we use two principles called Kirchhoff's rules:
- **1. Junction rule.** The sum of the currents entering any junction in a circuit must equal the sum of the currents leaving that junction:

$$\sum I_{\text{in}} = \sum I_{\text{out}}$$



- **2. Loop rule.** The sum of the potential differences across all elements around any closed circuit loop must be zero:

$$\sum_{\text{closed loop}} \Delta V = 0$$


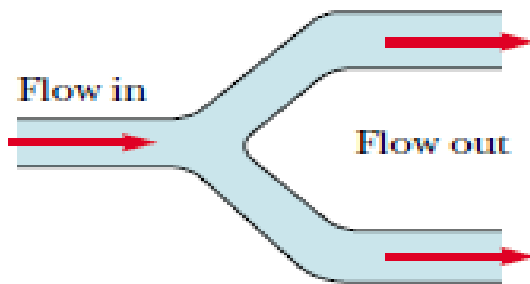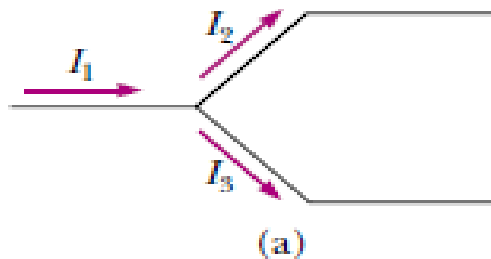
# Kirchhoff's Rules


- **Kirchhoff's first rule is a statement of conservation of electric charge.**
- All charges that enter a given point in a circuit must leave that point because charge cannot build up at a point.
- If we apply this rule to the junction shown in Figure, we obtain



$$I_1 = I_2 + I_3$$

When applying **Kirchhoff's second rule** in practice, we imagine *traveling* around the loop and consider changes in *electric potential*, rather than the changes in *potential energy* described in the preceding paragraph. You should note the following sign conventions when using the second rule:

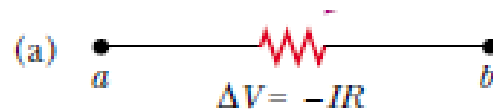
- Because charges move from the high-potential end of a resistor toward the low potential end, if a resistor is traversed in the direction of the current, the potential difference  $\Delta V$  across the resistor is  $-IR$ .



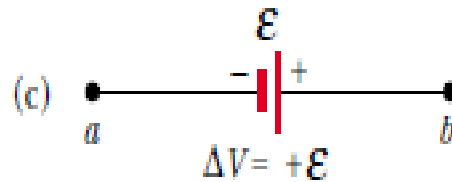
- If a resistor is traversed in the direction *opposite* the current, the potential difference  $\Delta V$  across the resistor is  $+IR$ .










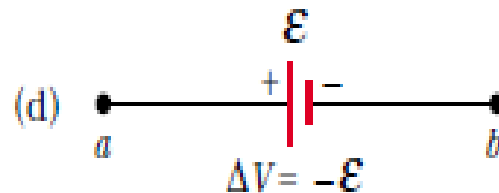
•If a source of emf (assumed to have zero internal resistance) is traversed in the **DIRECTION** of the emf (from - to +), the potential difference  $\Delta V$  is  $+\mathcal{E}$ . The emf of the battery increases the electric potential as we move through it in this direction.



•If a source of emf (assumed to have zero internal resistance) is traversed in the direction **OPPOSITE** the emf (from + to -), the potential difference  $\Delta V$  is  $-\mathcal{E}$ . In the case of the emf of the battery reduces the electric potential as we move through it.




# Circuit Analysis Conventions

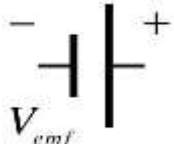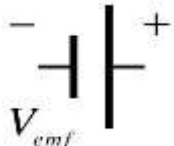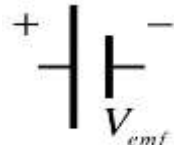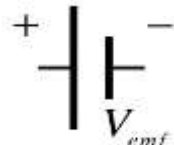Element	Analysis Direction	Current Direction	Voltage Drop
 <i>R</i>	→	→	$-iR$
 <i>R</i>	←	→	$+iR$
 <i>R</i>	→	←	$+iR$
 <i>R</i>	←	←	$-iR$
 $V_{emf}$	→		$+V_{emf}$
 $V_{emf}$	←		$-V_{emf}$
 $V_{emf}$	→		$-V_{emf}$
 $V_{emf}$	←		$+V_{emf}$

- Solve the circuit:

$$V = I_1 R_1 \Rightarrow I_1 = \frac{V}{R_1}$$
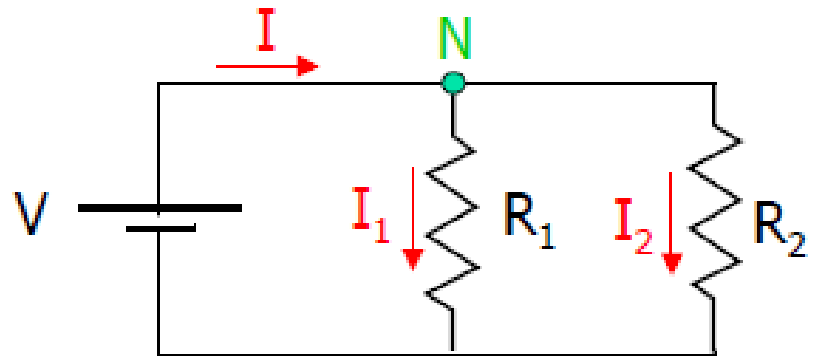
$$V = I_2 R_2 \Rightarrow I_2 = \frac{V}{R_2}$$



- Apply Kirchhoff's first law:  $I = I_1 + I_2$

$$I = I_1 + I_2 = V \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

## Example - Kirchoff's Laws

- At junction **b** the incoming current must equal the outgoing current

$$i_2 = i_1 + i_3$$


- At junction **a** we again equate the incoming current and the outgoing current

$$i_1 + i_3 = i_2$$

- But this equation gives us the same information as the previous equation!

- We need more information

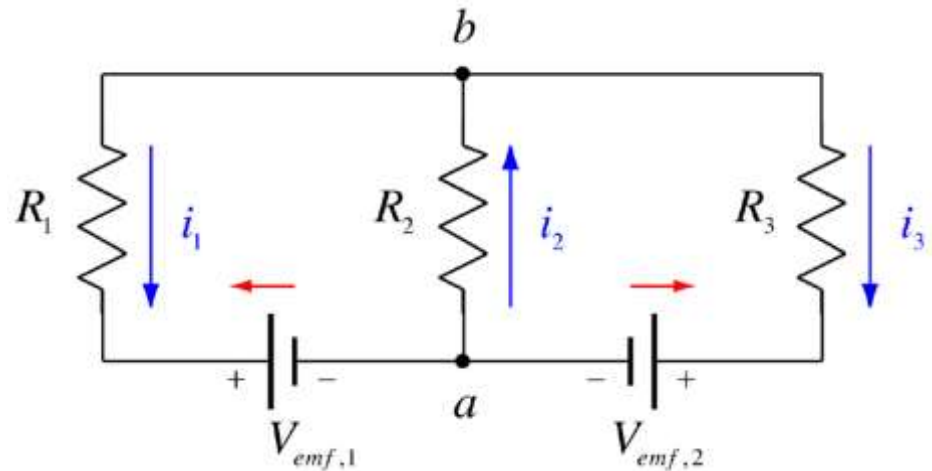to determine the three currents – 2 more independent equations



- We now have three equations


$$i_1 + i_3 = i_2 \quad i_1 R_1 + V_{emf,1} + i_2 R_2 = 0 \quad i_3 R_3 + V_{emf,2} + i_2 R_2 = 0$$

- And we have three unknowns  $i_1$ ,  $i_2$ , and  $i_3$
- We can solve these three equations in a variety of ways

$$i_1 = -\frac{(R_2 + R_3)V_{emf,1} - R_2 V_{emf,2}}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$i_2 = -\frac{R_3 V_{emf,1} + R_1 V_{emf,2}}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$
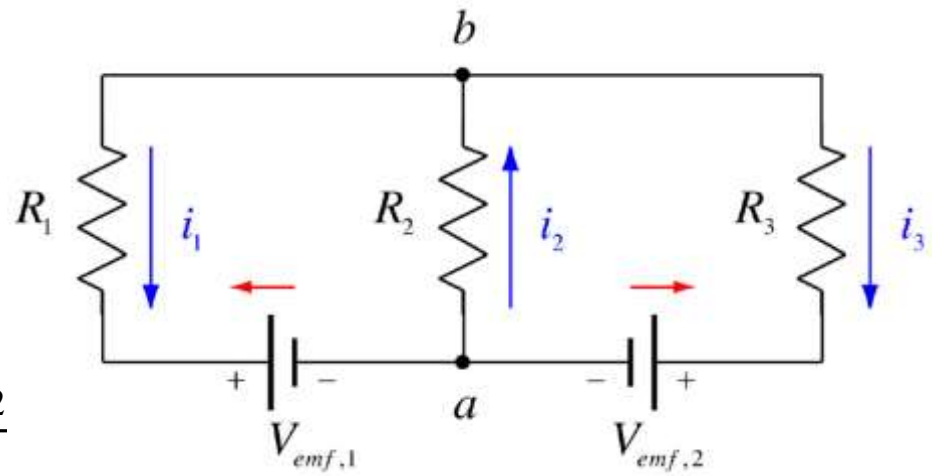
$$i_3 = -\frac{-R_2 V_{emf,1} + (R_1 + R_2)V_{emf,2}}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$



- Going around the left loop counterclockwise starting at point  $b$  we get
- Going around the right loop clockwise starting at point  $b$  we get


$$-i_1 R_1 - V_{emf,1} - i_2 R_2 = 0 \Rightarrow i_1 R_1 + V_{emf,1} + i_2 R_2 = 0$$

- Going around the outer loop clockwise starting at point  $b$  we get

$$-i_3 R_3 - V_{emf,2} - i_2 R_2 = 0 \Rightarrow i_3 R_3 + V_{emf,2} + i_2 R_2 = 0$$

- But this equation gives us no new information!


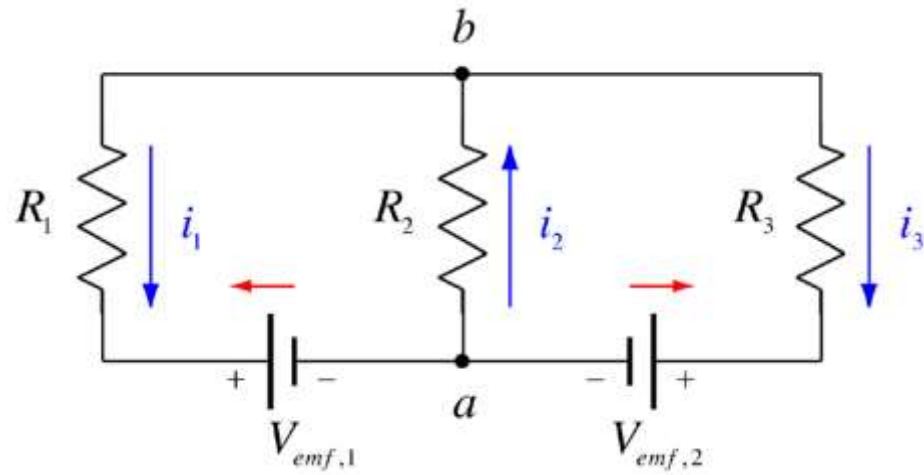
$$-i_3 R_3 - V_{emf,2} + V_{emf,1} + i_1 R_1 = 0$$




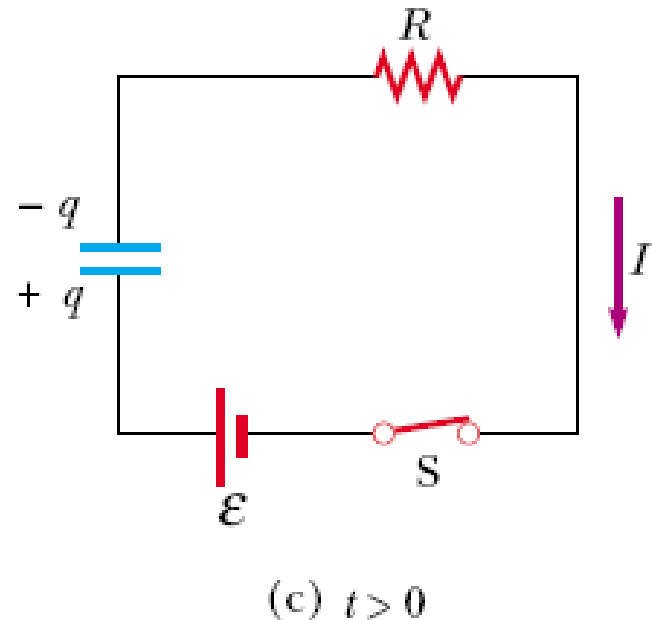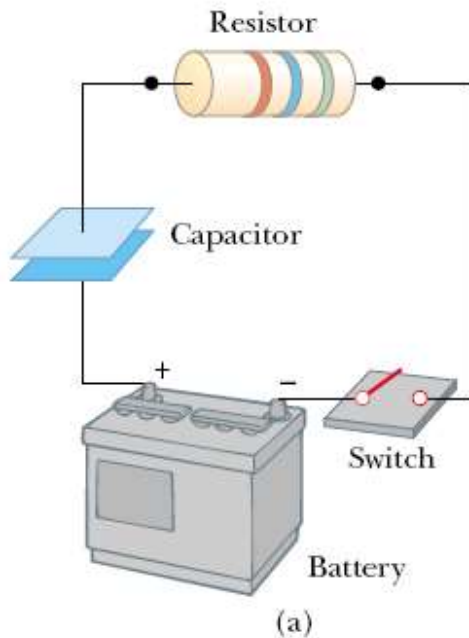
## Charging and Discharging Processes in RC Circuits

- A circuit containing a series combination of a resistor and a capacitor is called An **RC Circuits**




Circuit diagram

A capacitor in series with a resistor, switch, and battery.

## RC Circuits

- To analyze this circuit quantitatively, let us apply Kirchhoff's loop rule to the circuit after the switch is closed. Traversing the loop in Fig. c clockwise gives

$$\mathcal{E} - \frac{q}{C} - IR = 0$$

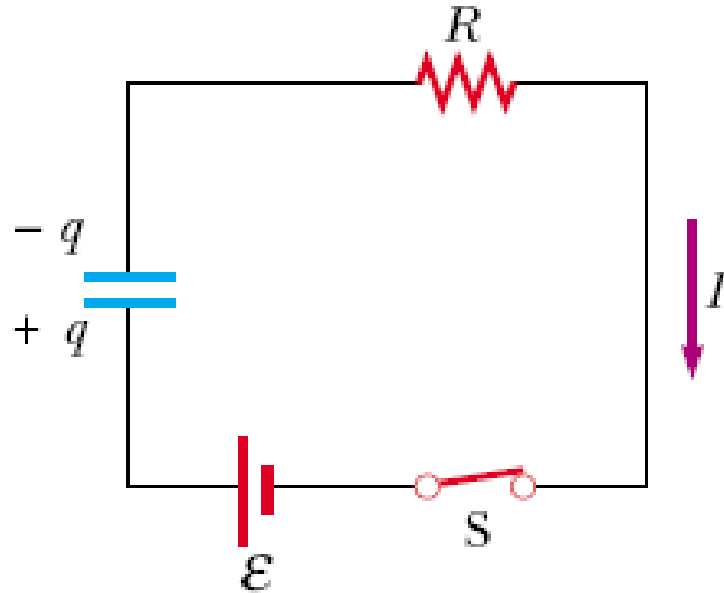

(c)  $t > 0$

where  $q/C$  is the potential difference across the capacitor and  $IR$  is the potential difference across the resistor.

# RC Circuits

- **Charging a Capacitor**

Charge as a function of time  
for a capacitor being charged

$$q(t) = C\mathcal{E} (1 - e^{-t/RC}) = Q(1 - e^{-t/RC})$$

**The charging current is**

$$I(t) = \frac{\mathcal{E}}{R} e^{-t/RC}$$

The quantity  $RC$ , which appears in the exponents of Equations, is called the time constant - of the circuit.

It represents the time interval during which the current decreases to  $1/e$  of its initial value.

# RC Circuits

- Discharging a Capacitor

Charge as a function of time for a discharging capacitor

$$q(t) = Qe^{-t/RC}$$

**Current as a function of time for a discharging capacitor:**

$$I(t) = \frac{dq}{dt} = \frac{d}{dt} (Qe^{-t/RC}) = -\frac{Q}{RC} e^{-t/RC}$$

where  $Q/RC = I_0$  is the initial current.

The negative sign indicates that as the capacitor discharges, the current direction is opposite its direction when the capacitor was being charged.