

# Lecture 7


## The Electric Current and the resistance

- **Introduction**
- **Electric current**
- **The Electromotive Force and Internal Resistance**
- **Electrical energy and thermal energy**
- **Resistors in series.**
- **Resistors in parallel.**
- **Kirchhoff's Laws and its applications.**
- **Charging and Discharging Processes in RC**

## Introduction

The results of the last two chapters (particularly those involving conductors) apply to the special case that electric charges are not in motion, **the electrostatic case**. For that case, all the points of a single conductor were at **the same potential** and the electric field was **zero** within the material of the conductor. In certain situations, we can maintain **the motion of charges** through a conductor, as when we connect a battery across the ends of a wire. In that case electric charge (negative charge, as it turns out) moves through the wire and there will be potential differences between the points of the conductor.
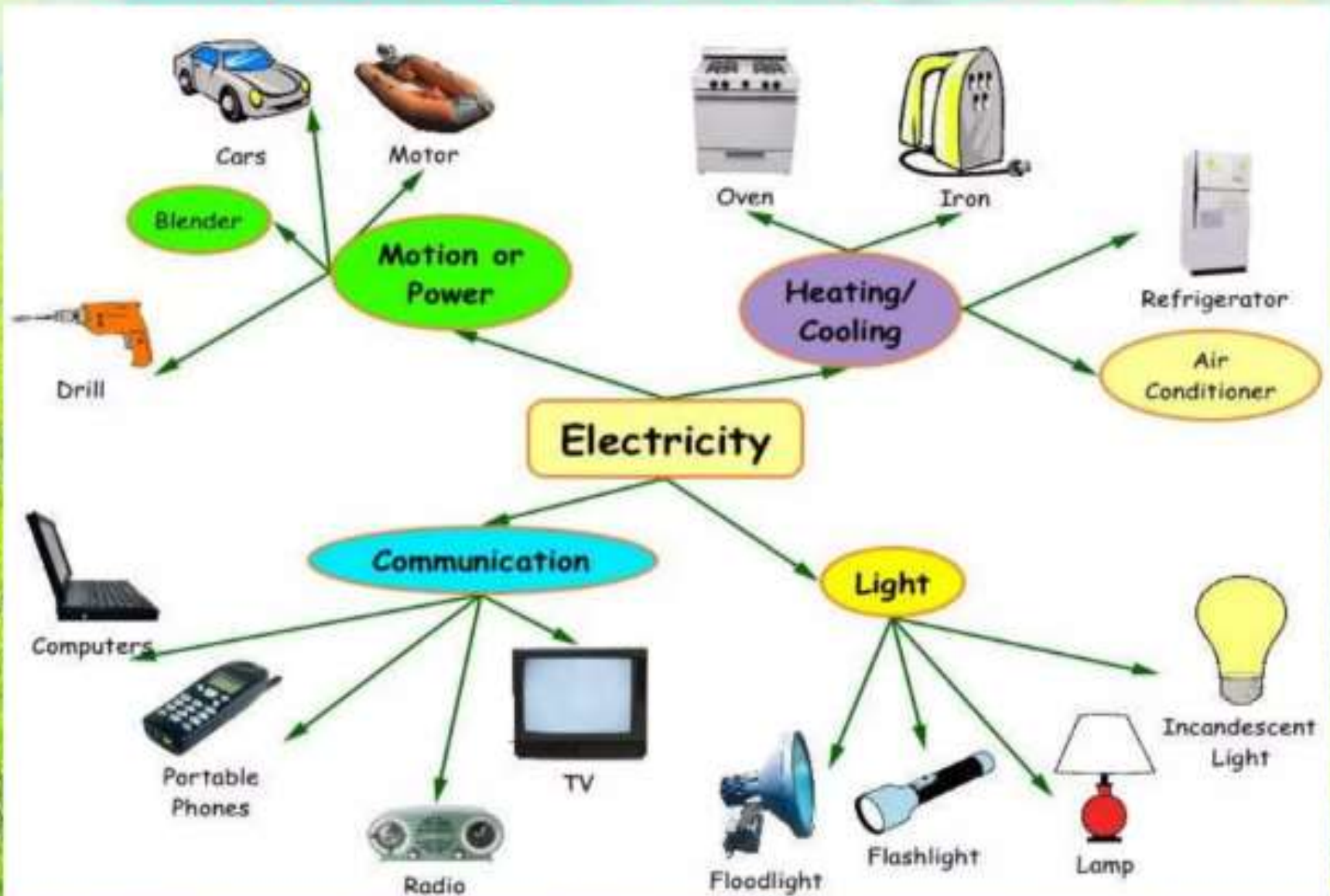
# Electricity is a form of a energy that can be easily changed to many other forms




# Electric current

The **current** is defined as the **flow of the charge**.

- The current is the rate at which charge flows through a surface of area  $A$ ,
- If  $\Delta Q$  is the amount of charge that passes through this area in a time interval  $\Delta t$ , the average current  $I_{av}$  is equal to the charge that passes through  $A$  per unit time:

$$I_{av} = \frac{\Delta Q}{\Delta t}$$

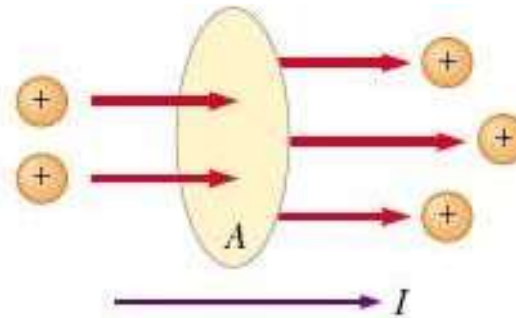

The SI unit of current is the ampere (A): That is, 1 A of current is equivalent to 1 C of charge passing through the surface area in 1 s.

$$1 \text{ A} = \frac{1 \text{ C}}{1 \text{ s}}$$



# The current density

Consider a conductor of cross-sectional area  $A$  carrying a current  $I$ . The current density  $\mathbf{J}$  in the conductor is defined as the current per unit area. Because the current  $I = nqv_d A$ , the current density is

**The current density** 
$$\mathbf{J} \equiv \frac{I}{A} = nqv_d$$

where  $\mathbf{J}$  has SI units of  $\text{A/m}^2$ .


A current density  $\mathbf{J}$  and an electric field  $\mathbf{E}$  are established in a conductor, whenever a potential difference is maintained across the conductor, the current density is proportional to the electric field:

$$\mathbf{J} = \sigma \mathbf{E}$$


$\sigma$  is called the conductivity of the conductor.
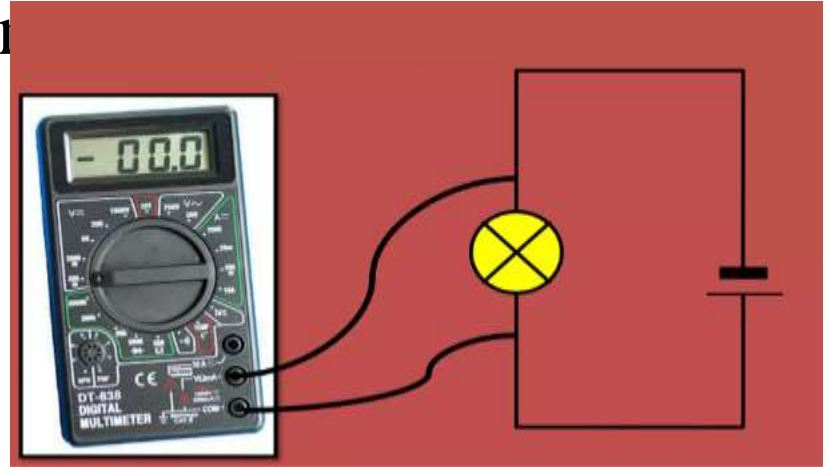
# Electric potential and potential difference

**Electric potential**-work done in 1 from infinity to a point.



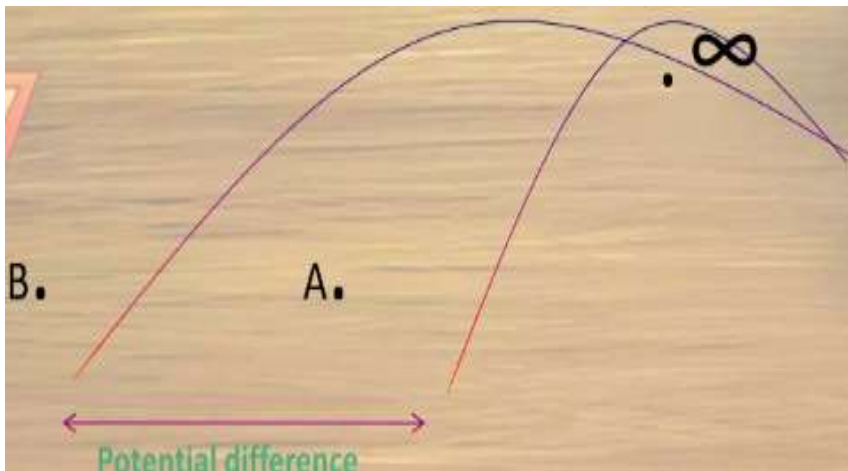**Potential Difference**-The difference between potential at two points.



# Electromotive Force, emf

- **Electromotive force** is the same as voltage
- When the current in the circuit is constant in magnitude and direction and is called **direct current DC**.
- A battery is called a source of electromotive force or, *emf*.
- The emf of a battery is the maximum possible voltage that the battery can provide between its terminals.
- When an electric potential difference exists between two points, the source moves charges from the lower potential to the higher.



# Ohm's Law

- For many substances it is found that the current flowing through a wire made of the material is proportional to the potential difference across its ends:  $I \propto V$  . We write this relation in the following way:

$$\frac{V}{I} = R \quad \text{or} \quad V = IR$$

- where  $R$  is constant which depends on the properties of the wire (its material and its dimensions).  $R$  is called the resistance of the wire and this relation is known.
- From the relation  $R = V/I$  we see that the units of resistance must  $\frac{V}{A}$  be. This combination of units is called an ohm:  
The unit of resistance is Ohms ( $\Omega$ ):  $1 \Omega = 1 \text{ V/A}$ 
$$1 \text{ ohm} = 1 \Omega = 1 \frac{V}{A}$$





# The internal resistance

- The resistance of the battery is called **internal resistance**  $r$ .
- $I$  is the current in the circuit,  $I_r$  is the current through the resistor, emf is  $\varepsilon$
- The terminal voltage of the battery

$$\Delta V = V_b - V_a \text{ is}$$

$$\Delta V = \varepsilon - I_r$$

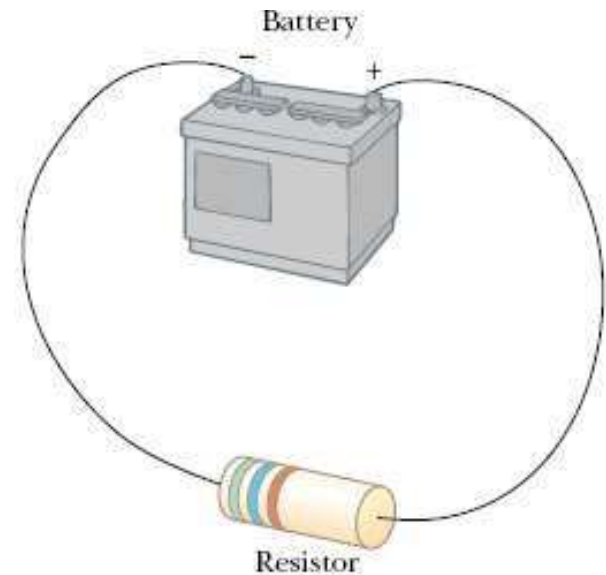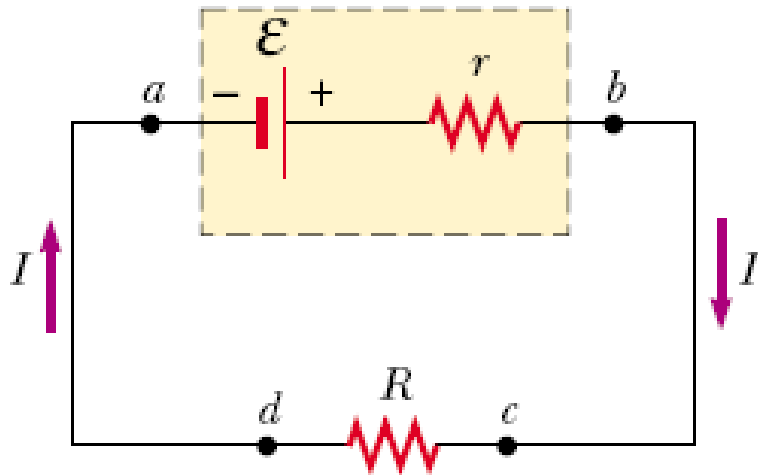

## Resistance and Resistivity

The resistance of a piece of material depends on the type and shape of the material. If the piece has length  $L$  and cross-sectional area  $A$ , the resistance is  $R = \rho \frac{L}{A}$

where  $\rho$  is a constant (for a given material at a given

$$\rho_{\text{Copper}} = 1.72 \times 10^{-8} \Omega \cdot \text{m} \quad \rho_{\text{Aluminum}} = 2.82 \times 10^{-8} \Omega \cdot \text{m} \quad \rho_{\text{Carbon}} = 3.5 \times 10^{-5} \Omega \cdot \text{m}$$

selected values for  $\rho$  are:

The resistivity of a material usually increases with temperature. It generally follows an empirical formula given by:


$$\rho = \rho_0[1 + \alpha(T - T_0)]$$

## Example 1

A cylindrical copper cable carries a current of 1200 A. There is a potential difference of  $1.6 \times 10^{-2} \text{ V}$  between two points on the cable that are 0.24 m apart.

What is the radius of the cable?

## Solution

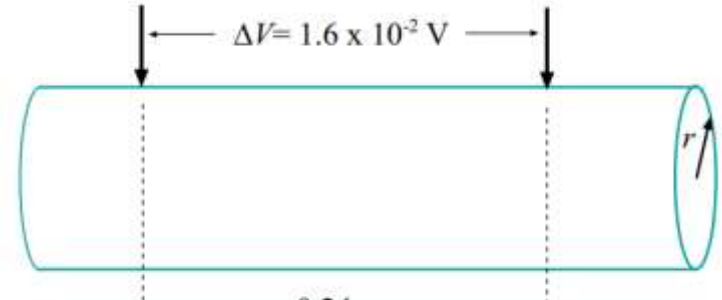

$$R = \frac{V}{I} = \frac{(1.6 \times 10^{-2} \text{ V})}{(1200 \text{ A})} = 1.33 \times 10^{-5} \Omega$$

Then from Eq. 4.6, knowing  $R$ ,  $L$  and the resistivity of the material (i.e. copper) we can get the cross-sectional area:

$$R = \rho \frac{L}{A} \quad \Rightarrow \quad A = \frac{\rho L}{R}$$

Plug in the numbers:

$$A = \frac{(1.72 \times 10^{-8} \Omega \cdot \text{m})(0.24 \text{ m})}{(1.33 \times 10^{-5} \Omega)} = 3.10 \times 10^{-4} \text{ m}^2$$

The cable has a circular cross-section so that  $A = \pi r^2$ . Solve for  $r$ :

$$r^2 = \frac{A}{\pi} = 9.87 \times 10^{-5} \text{ m}^2 \quad \Rightarrow \quad r = 9.93 \times 10^{-3} \text{ m} = 9.93 \text{ mm}$$

**Table 5.1 Values of Resistivity of Materials**

| <b>Material</b>        | <b>Resistivity (<math>\Omega \cdot \text{m}</math>)</b> |
|------------------------|---|
| <b>Metals:</b>         |   |
| Silver                 | $1.47 \times 10^{-8}$                                   |
| Copper                 | $1.72 \times 10^{-8}$                                   |
| Gold                   | $2.44 \times 10^{-8}$                                   |
| Aluminum               | $2.63 \times 10^{-8}$                                   |
| Tungsten               | $5.51 \times 10^{-8}$                                   |
| Steel                  | $20 \times 10^{-8}$                                     |
| Lead                   | $22 \times 10^{-8}$                                     |
| Mercury                | $95 \times 10^{-8}$                                     |
| <b>Semiconductors:</b> |   |
| Pure carbon            | $3.5 \times 10^{-5}$                                    |
| Pure germanium         | 0.60  |
| Pure silicon           | 2300  |
| <b>Insulators:</b>     |   |
| Amber                  | $5 \times 10^{14}$                                      |
| Mica                   | $10^{11} - 10^{15}$                                     |
| Teflon                 | $10^{16}$   |
| Quartz                 | $7.5 \times 10^{17}$                                    |

# Electrical Power and Electrical Work

All electrical circuits have three parts in common.

1. A voltage source.
  2. An electrical device
  3. Conducting wires.
- **The work done** (W) by a voltage source is equal to the work done by the electrical field in an electrical device,

$$1. \text{ Work} = \text{Power} \times \text{Time}.$$

**The electrical potential** is measured in joules/coulomb and a quantity of charge is measured in coulombs, so the electrical work is measure in joules.

A joule/second is a unit of power called the watt.

$$2. \text{ Power} = \text{current} \times \text{potential}$$

Or, 
$$P = I V = I^2 R$$

- $\text{Energy} = \text{Power} / \text{Time}$

## Electric Power



As charge moves through the wires of an electric circuit, they lose electric potential energy. (When charge  $\Delta q$  moves through a potential difference  $V$ , it loses  $\Delta qV$  of potential energy.) The rate of energy loss is the power  $P$  delivered to the circuit elements,

$$P = \frac{\Delta qV}{\Delta t} = \frac{\Delta q}{\Delta t}V = IV$$


$$P = IV$$

Electric power is measured in joules per second, or watts:  $1 \text{ J s}^{-1} = 1\text{W}$ . (We have already met this unit when we considered mechanical work done per unit time in first-semester physics.) The energy goes into heating the resistor. Using Ohm's law, ( $V = IR$ , or  $I = V/R$ ) we can show that the power delivered to a circuit element of resistance  $R$  can also be written as
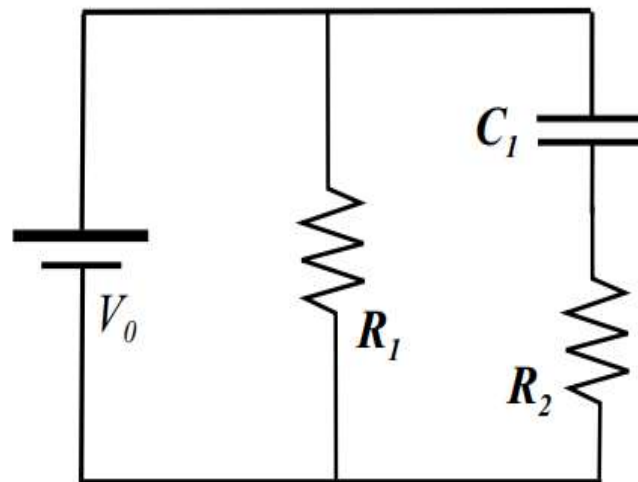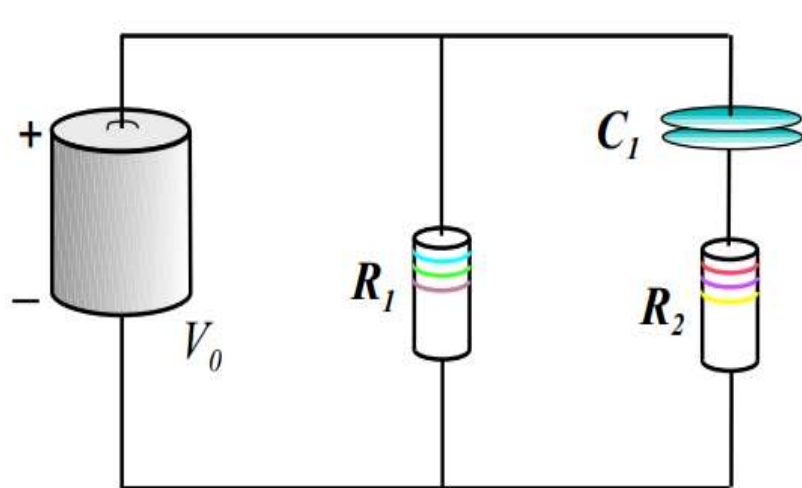
$$P = I^2R \quad \text{or} \quad P = \frac{V^2}{R}$$



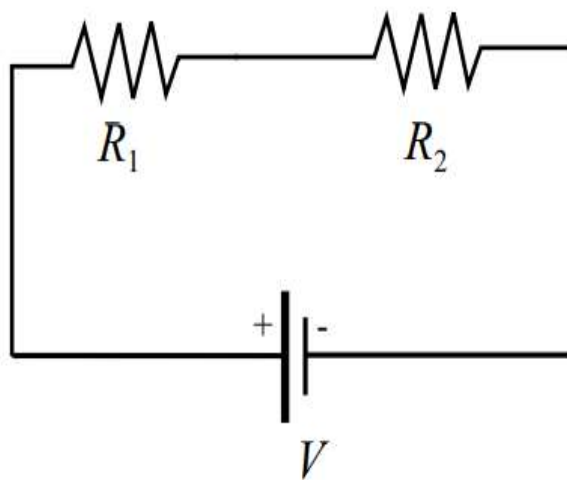
(a) Battery connected to two resistors and a capacitor. (b) Schematic diagram for this circuit.



Circuit with two resistors in series.



# Voltage sources

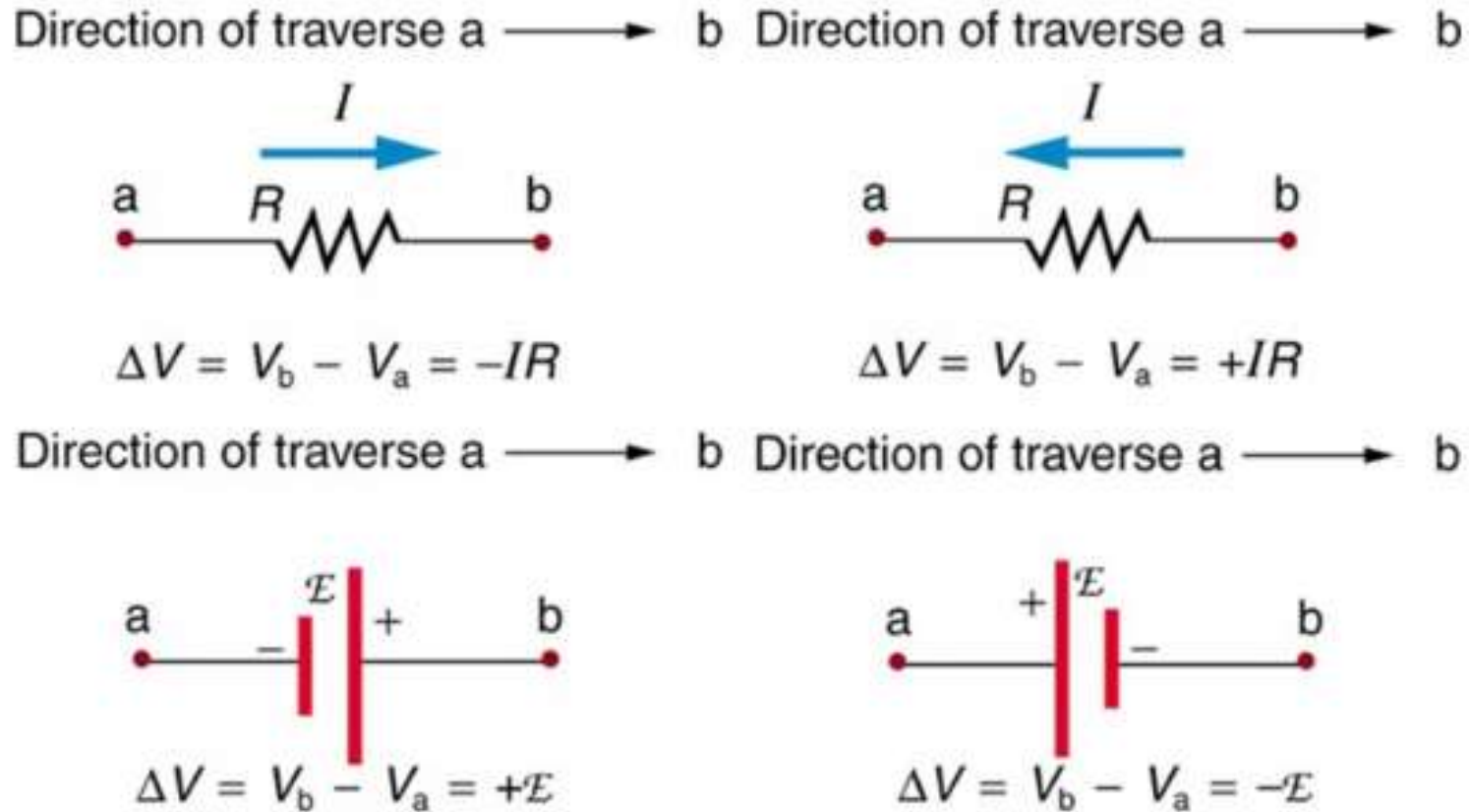

**Figure .** Each of these resistors and voltage sources is traversed from  $a$  to  $b$ . The potential changes are shown beneath each element and are explained in the text. (Note that the script  $\mathcal{E}$  stands for emf.)

## Electrical energy and thermal energy.

- The resistor represents a *load* on the battery because the battery must supply energy to operate the device.
- The potential difference across the load resistance is
- $\Delta V = \mathbf{IR}$  and

$$I = \frac{\mathcal{E}}{R + r}$$

- The total power output  $I \mathcal{E}$  of the battery is delivered to the external load resistance in the amount  $I^2 R$  and to the internal resistance in the amount  $I^2 r$ .

$$I\mathcal{E} = I^2 R + I^2 r$$

## Example 2

A battery has an emf of 12 V and an internal resistance of 0.05 Ohm. Its terminals are connected to a load resistance of 3.00 Ohm.

a- Find the current in the circuit and the terminal voltage of the battery.

### Solution

$$I = \frac{\mathcal{E}}{R + r} = \frac{12.0 \text{ V}}{3.05 \Omega} = 3.93 \text{ A}$$

We find the terminal voltage

$$\Delta V = \mathcal{E} - Ir = 12.0 \text{ V} - (3.93 \text{ A})(0.05 \Omega) = 11.8 \text{ V}$$




- Calculate the power delivered to the load resistor of 3 ohm when the current in the circuit is 3.93 A.

**Solution** The power delivered to the load resistor is

$$\mathcal{P}_R = I^2 R = (3.93 \text{ A})^2 (3.00 \Omega) = 46.3 \text{ W}$$
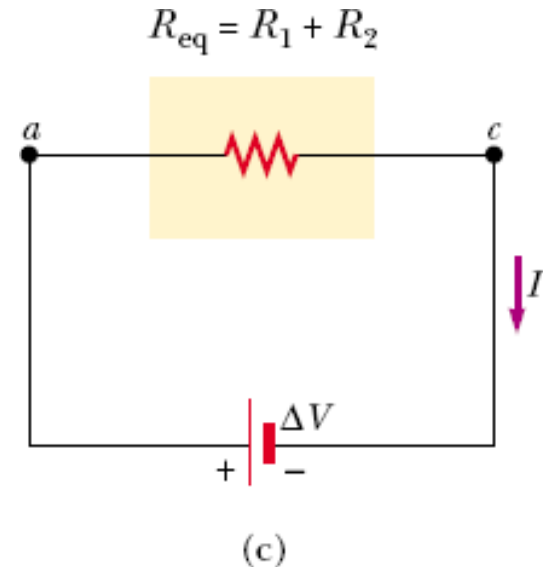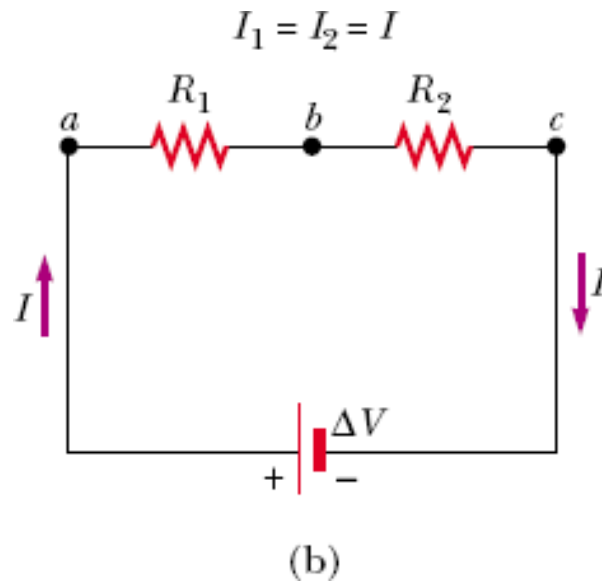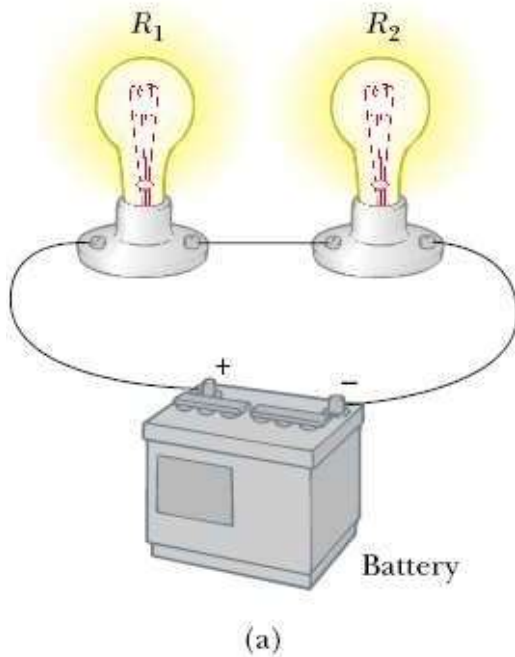
# Resistors in Series

- for a series combination of two resistors, the currents are the same in both resistors because the amount of charge that passes through  $R_1$  must also pass through  $R_2$  in the same time interval.



The potential difference across the battery is applied to the **equivalent resistance**  $R_{\text{eq}}$ :

$$\Delta V = IR_{\text{eq}}$$

# Resistors in Series

$$\Delta V = IR_{\text{eq}}$$


$$\Delta V = IR_{\text{eq}} = I(R_1 + R_2) \longrightarrow R_{\text{eq}} = R_1 + R_2$$

**The equivalent resistance of three or more resistors connected in series is**

$$R_{\text{eq}} = R_1 + R_2 + R_3 + \cdots$$

**Problem 5.8.** Consider the series portion of a circuit shown in Fig. 5-4. The current in the circuit flows from  $a$  to  $b$  and is 2.3 A.

- (a) What is the equivalent resistance?
- (b) What is the voltage across the entire circuit? Which point,  $a$  or  $b$ , is at the higher potential?
- (c) What is the voltage across each resistor?

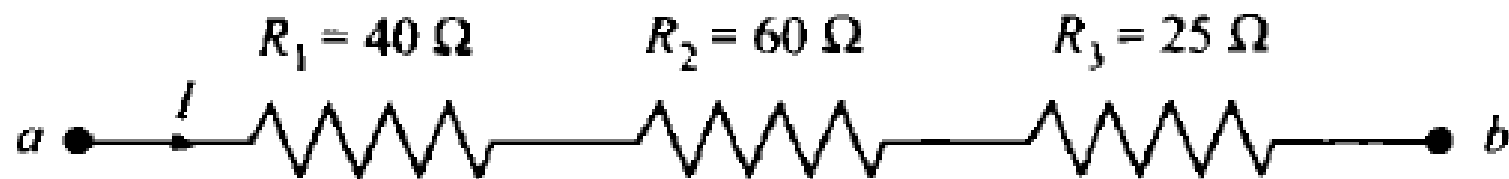

**Fig. 5-4**

**Problem 5.8.** Consider the series portion of a circuit shown in Fig. 5-4. The current in the circuit flows from  $a$  to  $b$  and is 2.3 A.

- (a) What is the equivalent resistance?
- (b) What is the voltage across the entire circuit? Which point,  $a$  or  $b$ , is at the higher potential?
- (c) What is the voltage across each resistor?

**Solution**



- (a) The equivalent resistance is the sum of all the resistances, or  $R_{eq} = 40 + 60 + 25 = 125 \Omega$ .
- (b) The voltage across the entire circuit is  $V_{total} = IR_{eq} = (2.3 \text{ A})(125 \Omega) = 288 \text{ V}$ . Since the current flows from  $a$  to  $b$ , and the electric field does positive work in pushing charges through the resistors, energy is lost as the charges move through. Thus the potential at  $a$  is higher (by 288 V) than the potential at  $b$ .
- (c) The voltage across each resistor is  $IR_i$ . Thus  $V_1 = (2.3 \text{ A})(40 \Omega) = 92 \text{ V}$ ,  $V_2 = (2.3 \text{ A})(60 \Omega) = 138 \text{ V}$  and  $V_3 = (2.3 \text{ A})(25 \Omega) = 58 \text{ V}$ .

*Note.* Adding the voltages gives  $92 + 138 + 58 = 288 \text{ V}$ , which is the voltage we calculated in part(b).


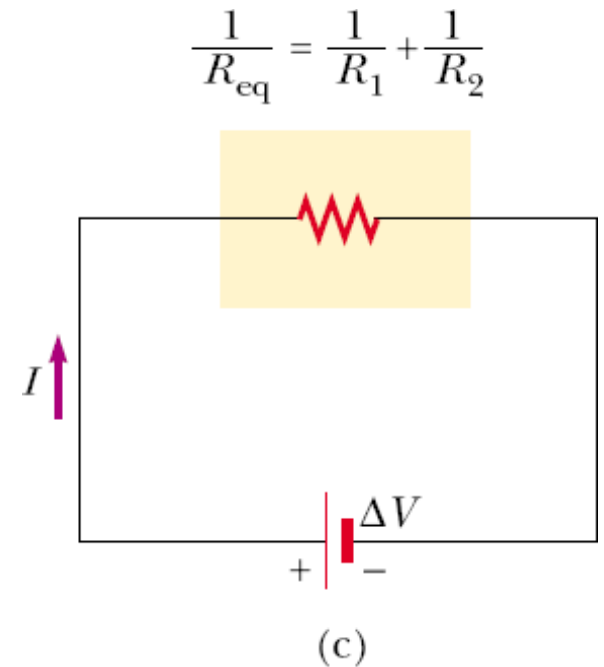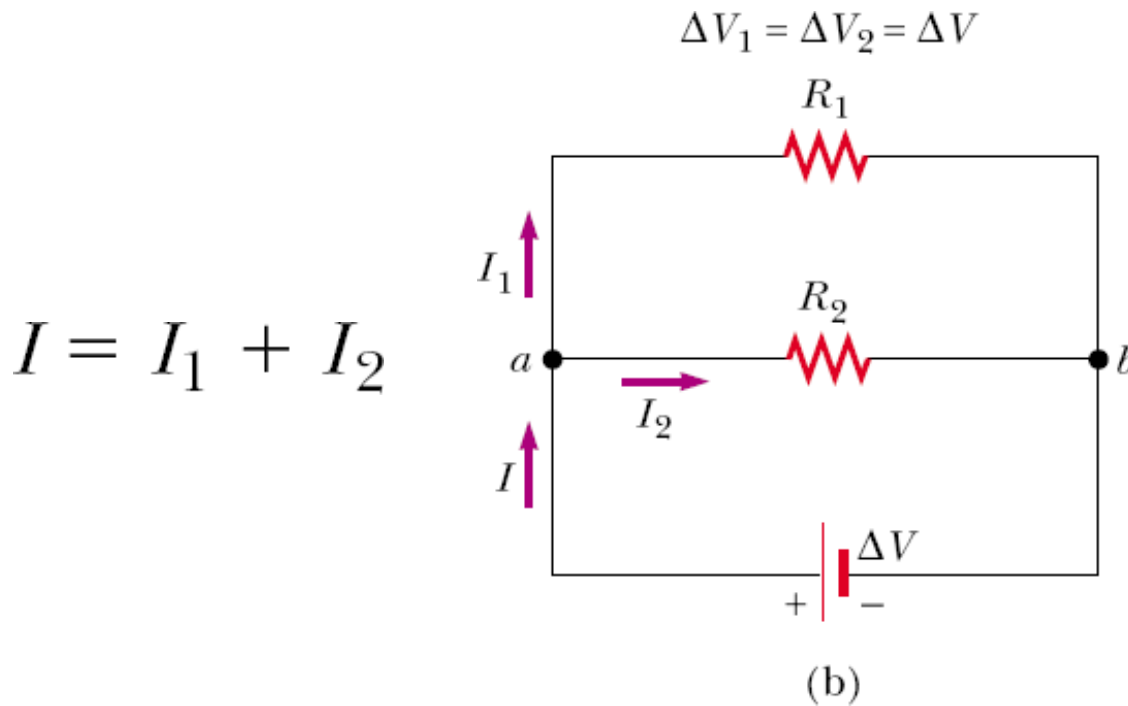
# Resistors in Parallel

- The current  $I$  that enters point  $a$  must equal the total current leaving that point:



When resistors are connected in parallel, the potential differences across the resistors **is the same**.

# Resistors in Parallel

- Because the potential differences across the resistors are the same, the expression
- $\Delta V = IR$  gives


$$I = I_1 + I_2 = \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2} = \Delta V \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{\Delta V}{R_{\text{eq}}}$$

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

the equivalent resistance
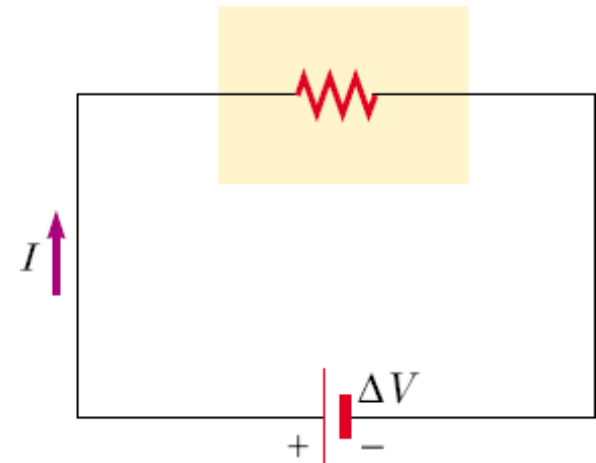
$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$




(c)

## Example

Three resistors are connected in parallel, The potential difference between a and b is 75 V.

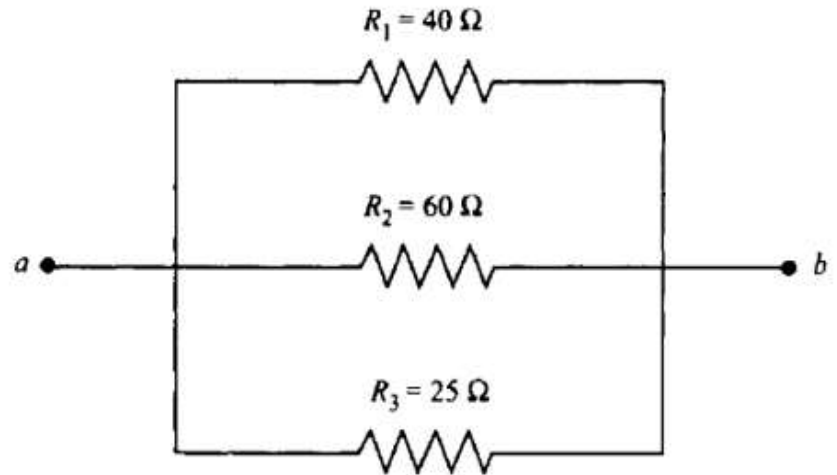
- a) What is the equivalent resistance of this circuit?
- a) What is the current flowing from point a?
- b) What is the current in each resistor?



### Solution

- (a) The equivalent resistance is given by  $1/R_{eq} = \Sigma (1/R_i) = 1/40 + 1/60 + 1/25 = 0.817$ , or  $R_{eq} = 12.2\ \Omega$ .
- (b) The total current is  $I_{tot} = V/R_{eq}$ . Thus  $I_{tot} = 6.13\ \text{A}$ .
- (c) The current in each resistor is  $I_i = V/R_i$ . Thus  $I_1 = (75\ \text{V})/(40\ \Omega) = 1.88\ \text{A}$ ,  $I_2 = (75\ \text{V})/(60\ \Omega) = 1.25\ \text{A}$ ,  $I_3 = (75\ \text{V})/(25\ \Omega) = 3.0\ \text{A}$ . [The total current is  $1.88 + 1.25 + 3.0 = 6.13\ \text{A}$ , as in part(b).]

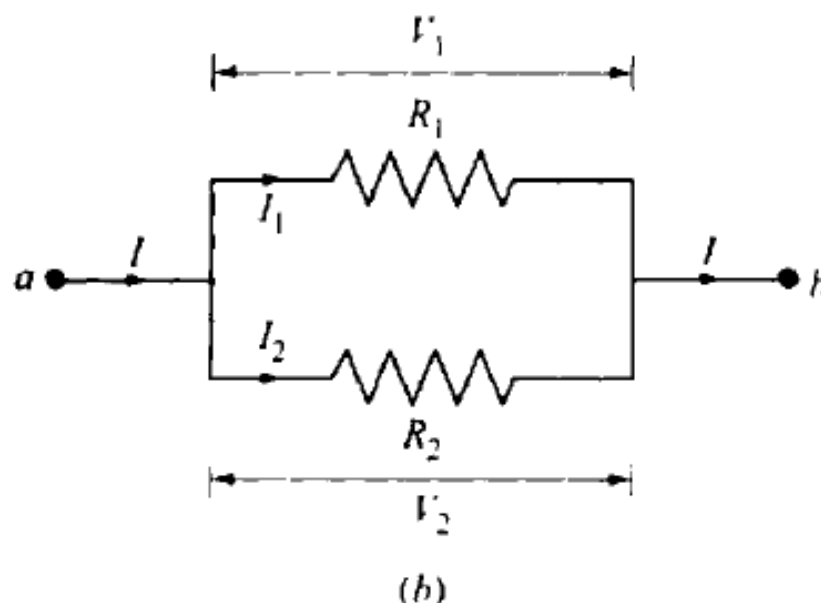**Problem 5.20.** In the circuit segment of Fig. 5-2(b), the voltage across the circuit is 55V. If  $R_1 = 25\ \Omega$  and  $R_2 = 35\ \Omega$ , calculate (a) the current in each resistor; (b) the power dissipated in each resistor and (c) the power dissipated in the equivalent resistance. Compare the answer to this with the sum of the answers to (b).



### Solution

(a) The voltage across each resistor is 55 V. Thus the current for each resistor is  $I = V/R$ . Then  $I_1 = (55\text{ V})/(25\ \Omega) = 2.2\text{ A}$ , and  $I_2 = (55\text{ V})/(35\ \Omega) = 1.57\text{ A}$ .

**Problem 5.20.** In the circuit segment of Fig. 5-2(b), the voltage across the circuit is 55V. If  $R_1 = 25\ \Omega$  and  $R_2 = 35\ \Omega$ , calculate (a) the current in each resistor; (b) the power dissipated in each resistor and (c) the power dissipated in the equivalent resistance. Compare the answer to this with the sum of the answers to (b).

### Solution

- (a) The voltage across each resistor is 55 V. Thus the current for each resistor is  $I = V/R$ . Then  $I_1 = (55\text{ V})/(25\ \Omega) = 2.2\text{ A}$ , and  $I_2 = (55\text{ V})/(35\ \Omega) = 1.57\text{ A}$ .
- (b) Since the voltage across each resistor is the same, the power in each resistor can be calculated using  $P = V^2/R$ . Thus  $P_1 = (55\text{ V})^2/(25\ \Omega) = 121\text{ W}$ , and  $P_2 = (55\text{ V})^2/(35\ \Omega) = 86.4\text{ W}$ . Alternatively, we could have used  $P = I^2R$ , using the current appropriate to each resistor. Then  $P_1 = (2.2\text{ A})^2(25\ \Omega) = 121\text{ W}$ , and  $P_2 = (1.57\text{ A})^2(35\ \Omega) = 86.4\text{ W}$ .
- (c) The equivalent resistance is  $R_{eq} = (25)(35)/(25 + 35) = 14.6\ \Omega$ . The total power is therefore  $P_{tot} = (55)^2/14.6 = 207.4\text{ W}$ . This equals the sum of  $P_1 + P_2 = 121 + 86.4$ .

# Kirchhoff's Rules

- The procedure for analyzing more complex circuits is greatly simplified if we use two principles called Kirchhoff's rules:
- **1. Junction rule.** The sum of the currents entering any junction in a circuit must equal the sum of the currents leaving that junction:



$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

- **2. Loop rule.** The sum of the potential differences across all elements around any closed circuit loop must be zero:

$$\sum_{\text{closed loop}} \Delta V = 0$$
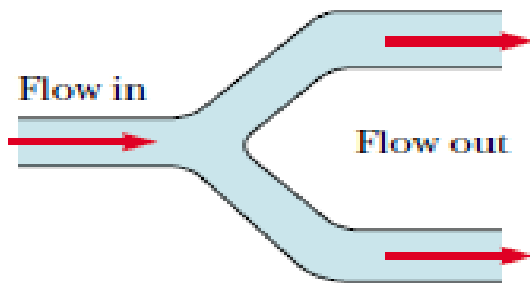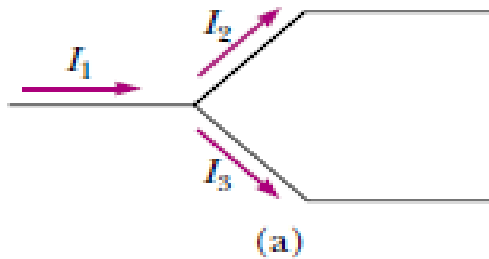
# Kirchhoff's Rules

- **Kirchhoff's first rule is a statement of conservation of electric charge.**
- All charges that enter a given point in a circuit must leave that point because charge cannot build up at a point.
- If we apply this rule to the junction shown in Figure, we obtain




$$I_1 = I_2 + I_3$$




When applying **Kirchhoff's second rule** in practice, we imagine *traveling* around the loop and consider changes in *electric potential*, rather than the changes in *potential energy* described in the preceding paragraph. You should note the following sign conventions when using the second rule: Because charges move from the high-potential end of a resistor toward the low potential end, if a resistor is traversed in the direction of the current, the potential difference  $\Delta V$  across the resistor is  $-IR$ .

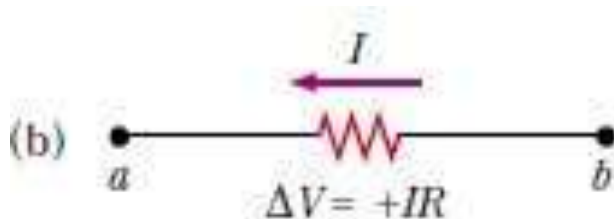
- If a resistor is traversed in the direction *opposite* the current, the potential difference  $\Delta V$  across the resistor is  $+IR$ .





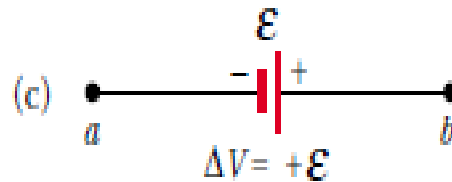•If a source of emf (assumed to have zero internal resistance) is traversed in the **DIRECTION** of the emf (from - to +), the potential difference  $\Delta V$  is  $+E$ . The emf of the battery increases the electric potential as we move through it in this direction.




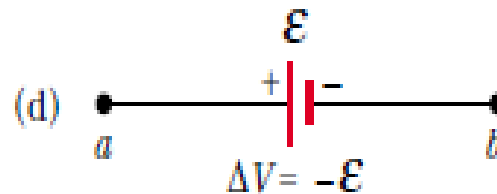•If a source of emf (assumed to have zero internal resistance) is traversed in the direction **OPPOSITE** the emf (from + to -), the potential difference  $\Delta V$  is  $-E$ . In the case of the emf of the battery reduces the electric potential as we move through it.



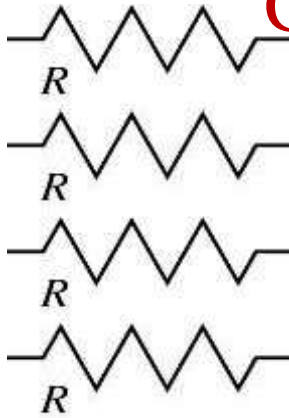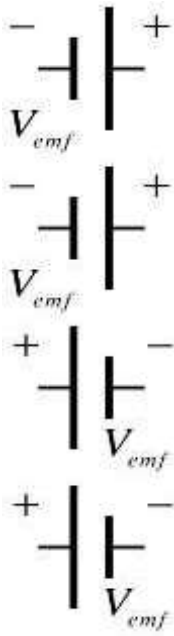
| Element  | Analysis Direction | Current Direction | Voltage Drop |
|--|--------------------|-------------------|--------------|
|   |                    |                   | $-iR$        |
|  | ←                  | →                 | $+iR$        |
|  | →                  | ←                 | $+iR$        |
|  | ←                  | ←                 | $-iR$        |
|  | →                  |                   | $+V_{emf}$   |
|  | ←                  |                   | $-V_{emf}$   |
|  | →                  |                   | $-V_{emf}$   |
|  | ←                  |                   | $+V_{emf}$   |

## Example

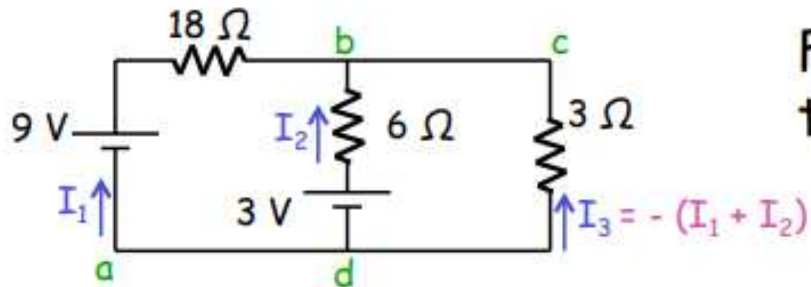

Find the current through each battery.

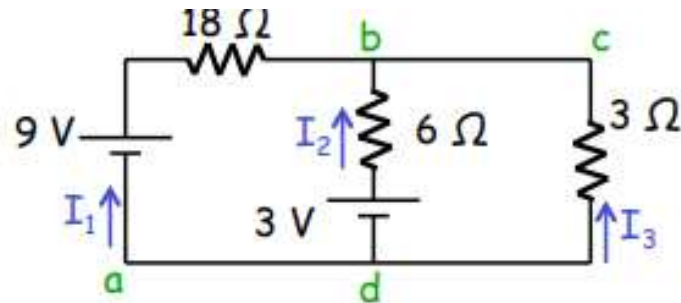The loop rule applied to loop *abda* will give:




- A)  $12A - 18I_1 + 6I_2 = 0$
- B)  $12A - 18I_1 - 6I_2 = 0$
- C)  $6A - 18I_1 - 6I_2 = 0$
- D)  $6A + 18I_1 + 6I_2 = 0$
- E)  $6A - 18I_1 + 6I_2 = 0$

- Solve the circuit:

$$V = I_1 R_1 \Rightarrow I_1 = \frac{V}{R_1}$$
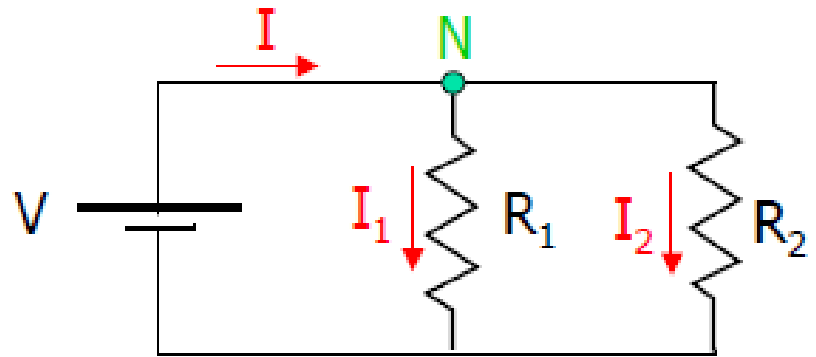
$$V = I_2 R_2 \Rightarrow I_2 = \frac{V}{R_2}$$



- Apply Kirchhoff's first law:  $I = I_1 + I_2$

$$I = I_1 + I_2 = V \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$

## Example - Kirchhoff's Rules

- At junction ***b*** the incoming current must equal the outgoing current


$$i_2 = i_1 + i_3$$

- At junction ***a*** we again equate the incoming current and the outgoing current

$$i_1 + i_3 = i_2$$

- But this equation gives us the same information as the previous equation!

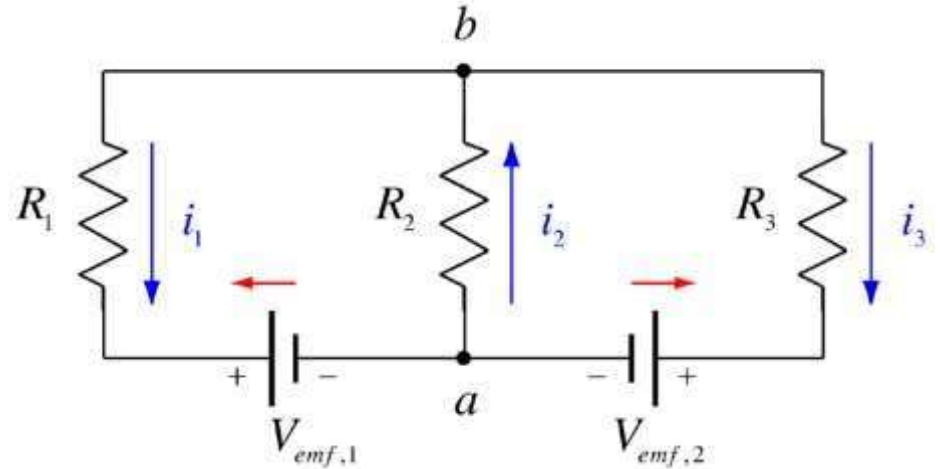- We need more information to determine the three currents – 2 more independent equations



- We now have three equations

$$i_1 + i_3 = i_2 \qquad i_1 R_1 + V_{emf,1} + i_2 R_2 = 0$$


- And we have three unknowns  $i_1$ ,  $i_2$ , and
- We can solve these three equations in :

$$i_1 = - \frac{(R_2 + R_3)V_{emf,1} - R_2 V_{emf,2}}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$i_2 = - \frac{R_3 V_{emf,1} + R_1 V_{emf,2}}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$i_3 = - \frac{-R_2 V_{emf,1} + (R_1 + R_2)V_{emf,2}}{R_1 R_2 + R_1 R_3 + R_2 R_3}$$

$$R_1 R_2 + R_1 R_3 + R_2 R_3$$

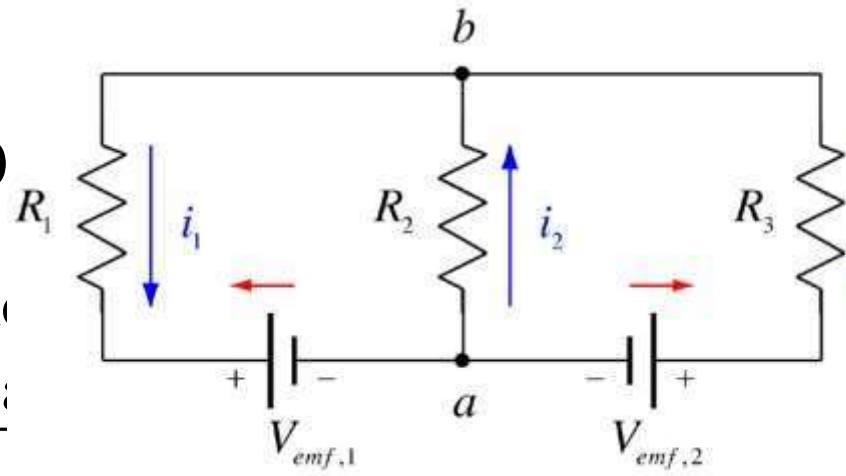



- Going around the left loop counterclockwise starting at point  $b$  we get
- Going around the right loop clockwise starting at point  $b$  we get


$$-i_1 R_1 - V_{emf,1} - i_2 R_2 = 0 \Rightarrow i_1 R_1 + V_{emf,1} + i_2 R_2 = 0$$

- Going around the outer loop clockwise starting at point  $b$  we get

$$-i_3 R_3 - V_{emf,2} - i_2 R_2 = 0 \Rightarrow i_3 R_3 + V_{emf,2} + i_2 R_2 = 0$$


- But this equation gives us no new information!
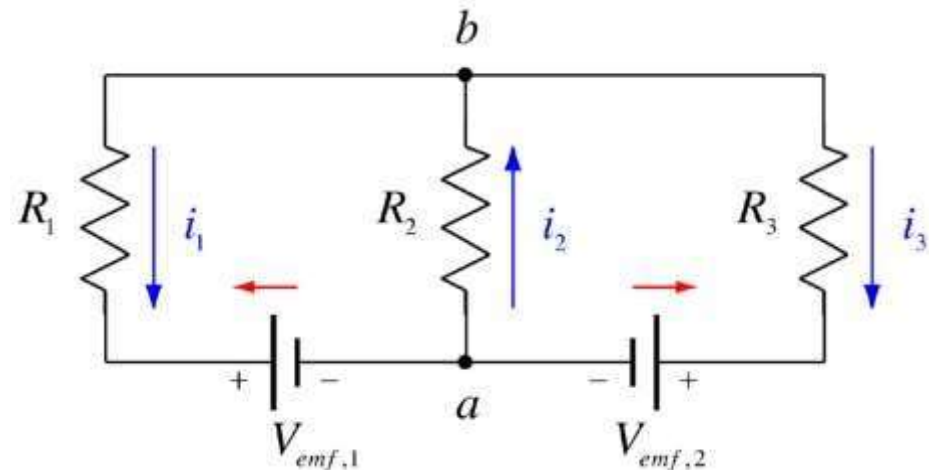
$$-i_3 R_3 - V_{emf,2} + V_{emf,1} + i_1 R_1 = 0$$


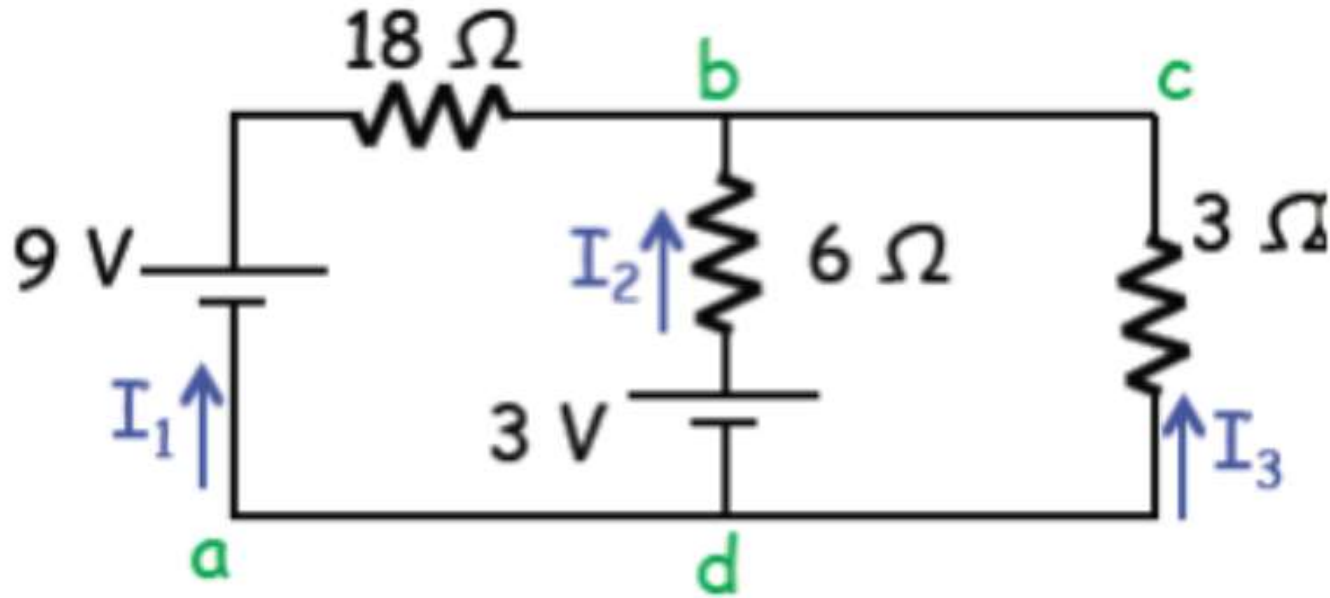
## Example

**Find** the current through each branch.



According to Kirchhoff's Current Law:

$$I_1 + I_2 + I_3 = 0 \dots\dots\dots \text{eq.1}$$

According to Kirchhoff's Voltage Law:

From loop 1:

$$9 \text{ V} = 18 I_1 - 6 I_2 + 3 \text{ V} \dots\dots\dots \text{eq.2}$$

From loop 2:

$$3 \text{ V} = 6 I_2 - 3 I_3 \dots\dots\dots \text{eq.3}$$

$$\text{eq.2} \Rightarrow 6 = 18 I_1 - 6 I_2 \Rightarrow I_1 = \frac{6+6I_2}{18} \Rightarrow I_1 = \frac{1+I_2}{3}$$

$$\text{eq.3} \Rightarrow 3 = 6 I_2 - 3 I_3 \Rightarrow I_3 = \frac{-3+6I_2}{3}$$

$$\begin{aligned} I_1 + I_2 + I_3 &= 0 \\ \Rightarrow \frac{1+I_2}{3} + I_2 + \frac{-3+6I_2}{3} &= 0 \\ \Rightarrow \frac{1+I_2+3I_2-3+6I_2}{3} &= 0 \Rightarrow I_2 = \frac{2}{10} \Rightarrow I_2 = 0.2 \text{ A} = 200 \text{ mA} \end{aligned}$$



$$I_1 = \frac{1+I_2}{3} \Rightarrow I_1 = \frac{1+0.2}{3} \Rightarrow I_1 = 0.4 \text{ A} = 400 \text{ mA}$$

$$I_3 = \frac{-3+6I_2}{3} \Rightarrow I_3 = \frac{-3+6 \times 0.2}{3} \Rightarrow I_3 = -0.6 \text{ A} = -600 \text{ mA}$$

**$I_3$ : is in the opposite direction:  $I_1 + I_2 = I_3$**
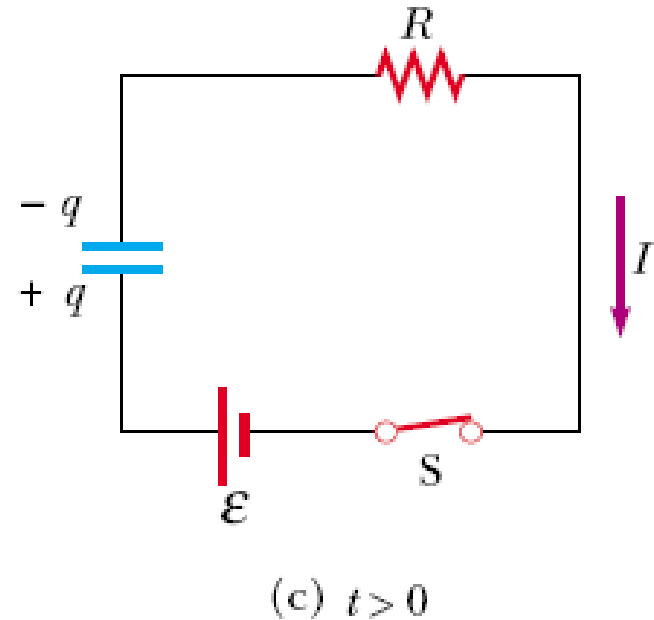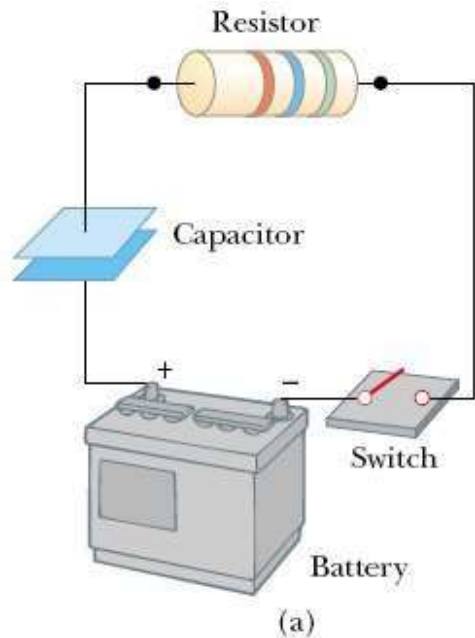
# Charging and Discharging Processes in RC Circuits

- A circuit containing a series combination of a resistor and a capacitor is called An **RC Circuits**




Circuit diagram

A capacitor in series with a resistor, switch, and battery.

## RC Circuits

- To analyze this circuit quantitatively, let us apply Kirchhoff's loop rule to the circuit after the switch is closed. Traversing the loop in Fig. c clockwise gives

$$\mathcal{E} - \frac{q}{C} - IR = 0$$

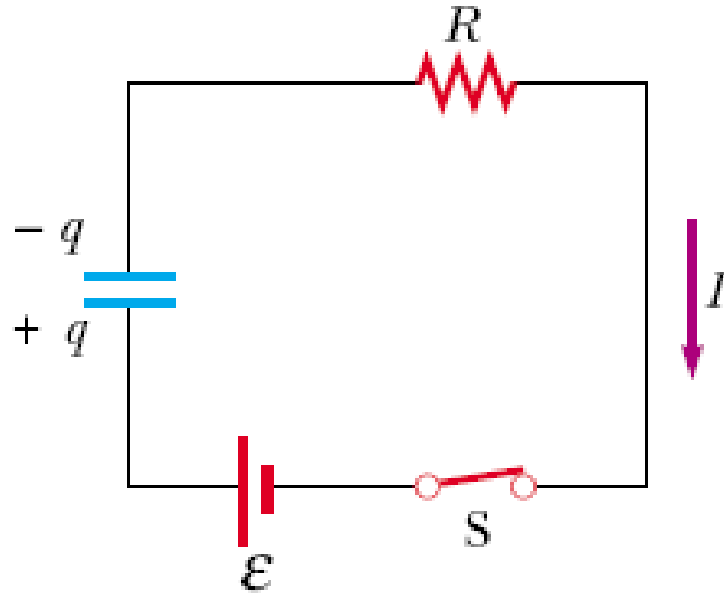

(c)  $t > 0$

where  $q/C$  is the potential difference across the capacitor and  $IR$  is the potential difference across the resistor.

# RC Circuits

- **Charging a Capacitor**

Charge as a function of time  
for a capacitor being charged

$$q(t) = C\mathcal{E}(1 - e^{-t/RC}) = Q(1 - e^{-t/RC})$$

**The charging current is**

$$I(t) = \frac{\mathcal{E}}{R} e^{-t/RC}$$

The quantity  $RC$ , which appears in the exponents of Equations, is called the time constant - of the circuit.

It represents the time interval during which the current decreases to  $1/e$  of its initial value.

# RC Circuits

- Discharging a Capacitor

Charge as a function of time for a discharging capacitor

$$q(t) = Qe^{-t/RC}$$

**Current as a function of time for a discharging capacitor:**

$$I(t) = \frac{dq}{dt} = \frac{d}{dt} (Qe^{-t/RC}) = -\frac{Q}{RC} e^{-t/RC}$$

where  $Q/RC = I_0$  is the initial current.

The negative sign indicates that as the capacitor discharges, the current direction is opposite its direction when the capacitor was being charged.