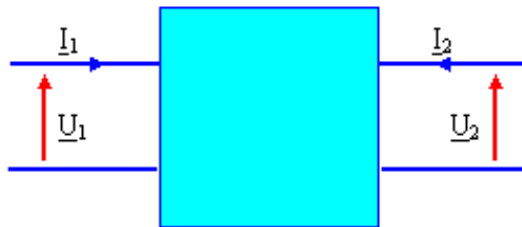
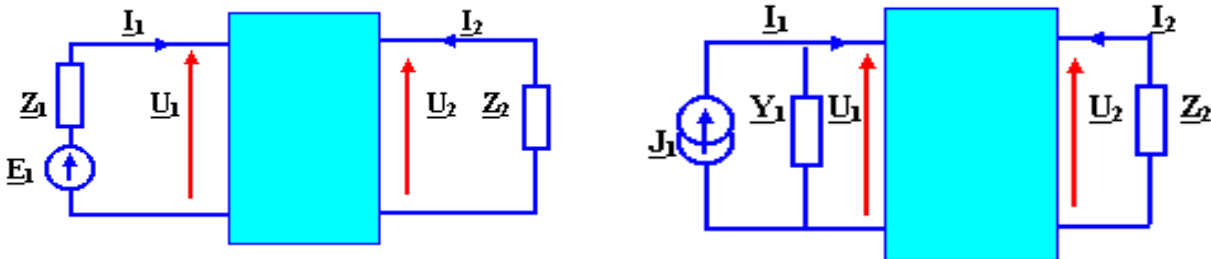


TP :1**Passive quadrupoles****I. Theoretical complement :****I.1) Definition :**

It's an electrical network with two inputs and two outputs, enabling the transfer of energy between two dipoles.

I.2) Representation :**I.3) Transfer function :**

Voltage gain: $\underline{F}_u = \underline{U}_2 / \underline{U}_1$

Current gain: $\underline{F}_i = \underline{I}_2 / \underline{I}_1$

Transfer admittance: $\underline{Y}_T = \underline{I}_2 / \underline{U}_1$

Transfer impedance: $\underline{Z}'_T = \underline{U}_2 / \underline{I}_1$

Input admittance: $\underline{Y}_e = \underline{I}_1 / \underline{U}_1$

Input impedance: $\underline{Z}'_e = \underline{U}_1 / \underline{I}_1$

I 4) Parameters :**1. Impedances:**

$$\underline{U}_1 = z_{11} \underline{I}_1 + z_{12} \underline{I}_2 .$$

$$\underline{U}_2 = z_{21} \underline{I}_1 + z_{22} \underline{I}_2 .$$

2. Admittances:

$$\underline{I}_1 = y_{11} \underline{U}_1 + y_{12} \underline{U}_2.$$

$$\underline{I}_2 = y_{21} \underline{U}_1 + y_{22} \underline{U}_2.$$

3. Hybrides (h):

$$\underline{U}_1 = h_{11} \underline{I}_1 + h_{12} \underline{U}_2.$$

$$\underline{I}_2 = h_{21} \underline{I}_1 + h_{22} \underline{U}_2.$$

4. Hybrides (g):

$$\underline{I}_1 = g_{11} \underline{U}_1 + g_{12} \underline{I}_2.$$

$$\underline{U}_2 = g_{21} \underline{U}_1 + g_{22} \underline{I}_2.$$


5. Transfert (T):

$$\underline{U}_1 = T_{11}\underline{U}_2 + T_{12} \underline{I}_2.$$


$$\underline{I}_1 = T_{21}\underline{U}_2 + T_{22} \underline{I}_2.$$

I.4) Propriétés of a passive quadripole:

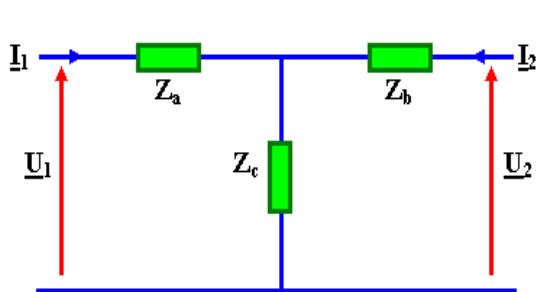Il est caractérisé par 3 paramètres. Il en résulte un diagramme équivalent T ou II.



the shape T

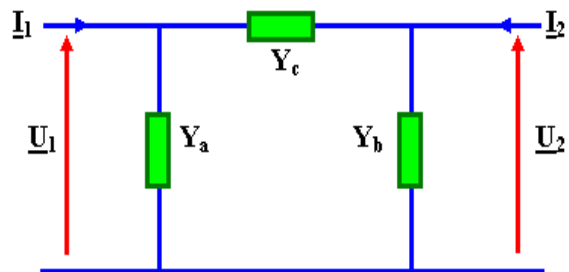

the shape II

Name and First name			Group	Grade
Name and First name				
Date : Schedule : Lab. N.....				

TP :1**Passive quadrupoles****I. Objectives:**


1. Set up the various circuits for measuring the currents and voltages required to determine the parameters of the Z, Y, h, g and T matrices of the two types of quadrupole: the "T" quadrupole and the "II" quadrupole.
2. Calculate these parameters from measured voltages and currents, then compare them with theoretical values.

I. Equipment used : The following equipment is required for this practical work :

- ☐ A stabilized power supply.
- ☐ A DC voltmeter.
- ☐ Two DC ampermeters.
- ☐ Connection cables.
- ☐ three $1\text{k}\Omega$ resistors.

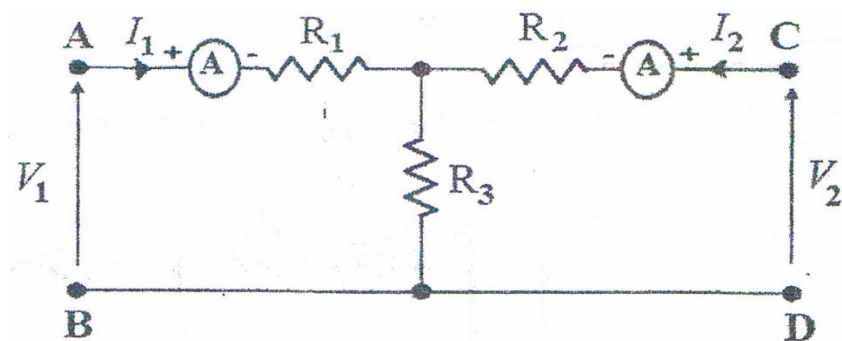
IV) Experimental study

➤ **"T" quadrupole:** create the following circuit:



- 1- Set ampermeters to 20 mA rating.
- 2- Connect a DC power supply between terminals A and B.
- 3- Set supply voltage to 10V and measure:


$V_1 =$
 $V_2 =$
 $I_1 =$
 $I_2 =$

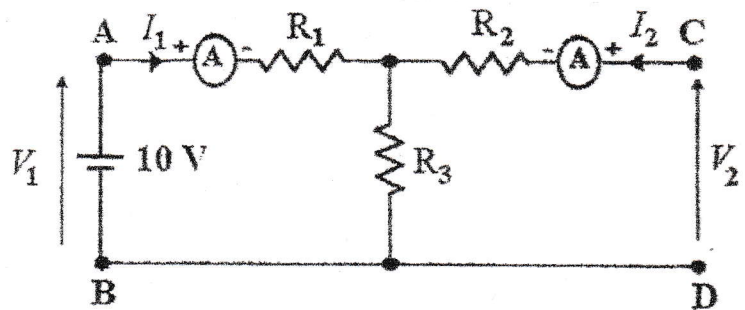

4- put a connecting cable between C and D and get the following circuit :

5- measure


$V_1 =$
 $I_1 =$
 $I_2 =$
 $V_2 =$

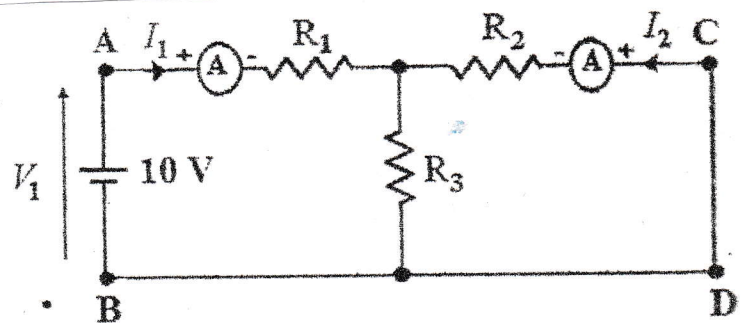

6- remove the connection cable

7- disconnect the power supply and connect it between C and D, obtaining the following circuit


$V_1 =$
 $V_2 =$
 $I_2 =$
 $I_1 =$

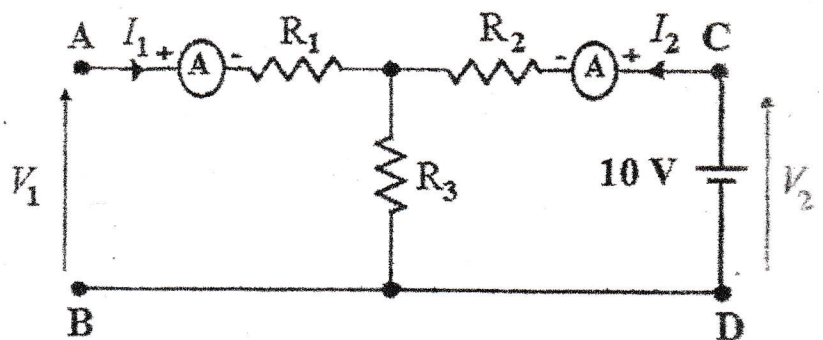

9- put a connecting cable between A and B and get the following circuit

10- measure

$V_2 =$
 $I_1 =$
 $I_2 =$
 $V_1 =$

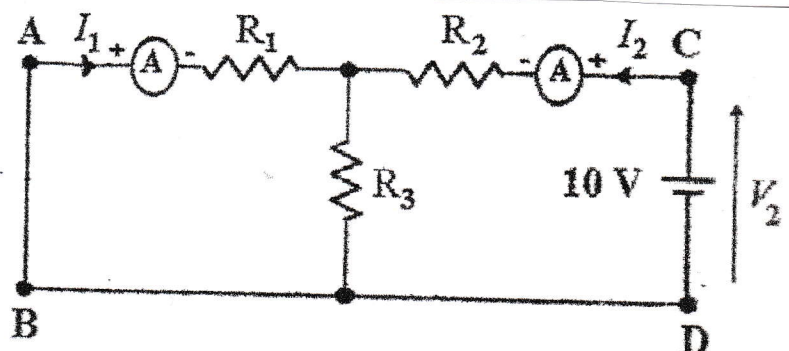

V) Calculation of matrices Z , Y , h , g and T :**V.1) Theoretical calculation of matrices parameters:**

Kirchhoff's laws are applied to determine the parameters of the various matrices as a function of the resistors R_1 , R_2 , R_3 :

➤ "T" quadrupole:**a) Z parameters :**

(give the theoretical expression)

(calculate numerical value)

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad Z_{11} = \dots \Rightarrow Z_{11} = \dots$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} \quad Z_{21} = \dots \Rightarrow Z_{21} = \dots$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} \quad Z_{12} = \dots \Rightarrow Z_{12} = \dots$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} \quad Z_{22} = \dots \Rightarrow Z_{22} = \dots$$

b) Y parameters : ($Y=Z^{-1}$)

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \quad Y_{11} = \dots \Rightarrow Y_{11} = \dots$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} \quad Y_{21} = \dots \Rightarrow Y_{21} = \dots$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} \quad Y_{12} = \dots \Rightarrow Y_{12} = \dots$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} \quad Y_{22} = \dots \Rightarrow Y_{22} = \dots$$

c) Parameters h :

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0} \quad h_{11} = \dots \Rightarrow h_{11} = \dots$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0} \quad h_{21} = \dots \Rightarrow h_{21} = \dots$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0} \quad \mathbf{h}_{12} = \dots \Rightarrow \mathbf{h}_{12} = \dots$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0} \quad \mathbf{h}_{22} = \dots \Rightarrow \mathbf{h}_{22} = \dots$$

d) The parameters g :

$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0} \quad \mathbf{g}_{11} = \dots \Rightarrow \mathbf{g}_{11} = \dots$$

$$g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0} \quad \mathbf{g}_{21} = \dots \Rightarrow \mathbf{g}_{21} = \dots$$

$$g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0} \quad \mathbf{g}_{12} = \dots \Rightarrow \mathbf{g}_{12} = \dots$$

$$g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0} \quad \mathbf{g}_{22} = \dots \Rightarrow \mathbf{g}_{22} = \dots$$

e) The parameters T :

$$T_{11} = \frac{V_1}{V_2} \Big|_{I_2=0} \quad \mathbf{T}_{11} = \dots 1 / \mathbf{g}_{21} \dots \Rightarrow \mathbf{T}_{11} = \dots$$

$$T_{21} = \frac{I_1}{V_2} \Big|_{I_2=0} \quad \mathbf{T}_{21} = \dots 1 / \mathbf{Z}_{21} \dots \Rightarrow \mathbf{T}_{21} = \dots$$

$$T_{12} = \frac{V_1}{I_2} \Big|_{V_2=0} \quad \mathbf{T}_{12} = \dots 1 / \mathbf{Y}_{21} \dots \Rightarrow \mathbf{T}_{12} = \dots$$

$$T_{22} = \frac{I_1}{I_2} \Big|_{V_2=0} \quad \mathbf{T}_{22} = \dots 1 / \mathbf{h}_{21} \dots \Rightarrow \mathbf{T}_{22} = \dots$$

V.2) Comparison of values found in practice with those found in theory :

- Using the measurements taken, determine the Z, Y, h, g and T matrices of quadrupole type 'T'.
- Remplir le tableau suivant.

	T-shaped quadrupole	
Matrices	Theoretical	Practice
Z parameters		
Y parameters		
h parameters		
g parameters		
T parameters		

VII) Discussion: discuss the results obtained

VIII Conclusion: draw an appropriate conclusion about this TP.
